

**For:sanjay**

**Printed on:Tue, Sep 22, 1998 14:03:00**

**Document:lab4**

**Last saved on:Tue, Sep 22, 1998 14:01:51**

# Lab 4: Complex gates and Static D flip-flop

## Introduction

The purpose of this lab is to familiarize the students with complex gates and the D flip-flop.

## Complex Gates

Set up the following complex gates in Hspice and verify their functionality:

$$Z = \text{not} ( A \text{ and } ((B \text{ and } C) \text{ or } D))$$
$$Z = \text{not}( A \text{ or } ((B \text{ or } C) \text{ and } D))$$

Obtain Z for all possible input combinations of ABCD for each complex gate above. Also obtain the plot of the inputs and the output Z for each gate. Use a separate panel to display each waveform but print out all the panels for each complex gate on a single page.

## D flip-flop

Set up a positive edge triggered static D flip-flop and verify its functioning.

Obtain the output Q for all possible combinations of CLK and D values. Show all the input and output waveforms on separate panels on a single page.

## Transistor sizes

Use minimum gate length of 0.6u for all transistors. Use 1.2u for the widths of all nmos transistors and 2.4u for the widths of pmos transistors. Use VDD = 3.3v.

## To Turn In

1. A schematic of your implementation of the complex gates and the D flip flop.  
(a neat hand drawn schematic is acceptable)
2. Your spice stimulus files and circuit files for each.
3. Mwave plots for each circuit as mentioned above.