

# Spring 2007 - Tutorial 1

## Analog Circuit Elements



**UW ASIC**  
design ♦ team

UW ASIC Design Team

June 17, 2007



# Outline

## Discrete Circuit Elements

The Resistor

The Capacitor

The Inductor

## Filters

Low-Pass Filters

High-Pass Filters

Bandpass Filters

Bandreject Filters

## Amplifiers

Operational Amplifiers


OpAmp-based Active Filters

Transistor Amplifiers

## PSpice Simulation




# The Resistor

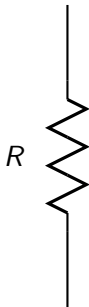

- ▶ I-V characteristics:  $V = IR$




# The Resistor

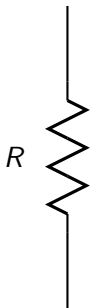


- ▶ I-V characteristics:  $V = IR$
- ▶ No frequency dependence

# The Resistor

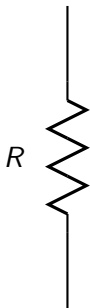


- ▶ I-V characteristics:  $V = IR$
- ▶ No frequency dependence
- ▶ Power dissipation:  $P = I^2R$

# The Resistor

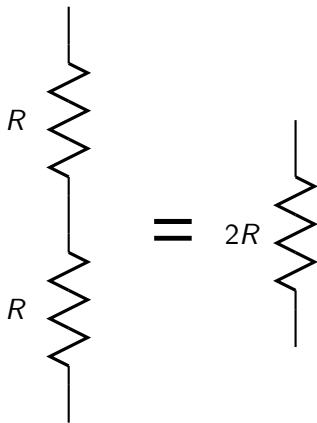


- ▶ I-V characteristics:  $V = IR$
- ▶ No frequency dependence
- ▶ Power dissipation:  $P = I^2R$
- ▶ Add in series

# The Resistor

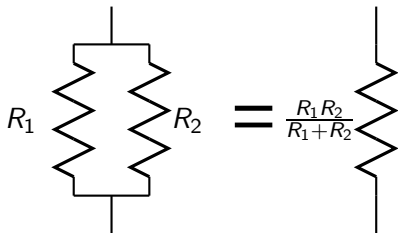

- ▶ I-V characteristics:  $V = IR$
- ▶ No frequency dependence
- ▶ Power dissipation:  $P = I^2 R$
- ▶ Add in series
- ▶ Inverse total equals inverse addition in parallel


# The Capacitor

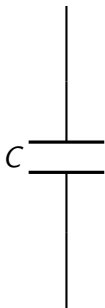

- ▶ I-V characteristics:  $I = C \frac{dV}{dt}$




# The Capacitor

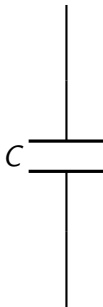


- ▶ I-V characteristics:  $I = C \frac{dV}{dt}$
- ▶ Frequency dependent impedance:  
 $Z = \frac{1}{j\omega C}$

# The Capacitor

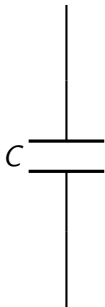


- ▶ I-V characteristics:  $I = C \frac{dV}{dt}$
- ▶ Frequency dependent impedance:  
 $Z = \frac{1}{j\omega C}$
- ▶ No power dissipation (ideally)

# The Capacitor

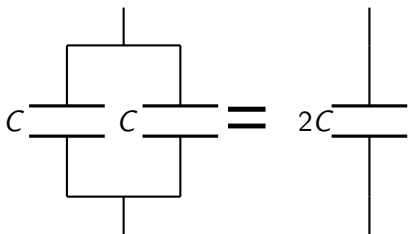


- ▶ I-V characteristics:  $I = C \frac{dV}{dt}$
- ▶ Frequency dependent impedance:  $Z = \frac{1}{j\omega C}$
- ▶ No power dissipation (ideally)
- ▶ Add in parallel

# The Capacitor

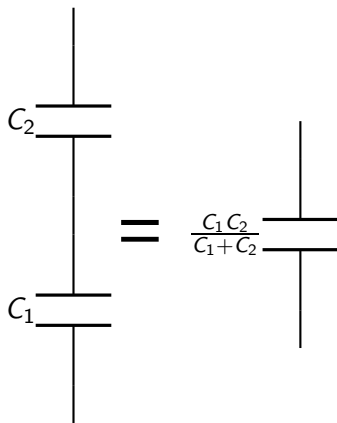


- ▶ I-V characteristics:  $I = C \frac{dV}{dt}$
- ▶ Frequency dependent impedance:  $Z = \frac{1}{j\omega C}$
- ▶ No power dissipation (ideally)
- ▶ Add in parallel
- ▶ Inverse total equals inverse addition in series

# The Inductor

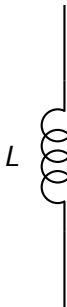


- ▶ I-V characteristics:  $V = L \frac{di}{dt}$

# The Inductor

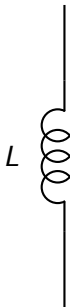


- ▶ I-V characteristics:  $V = L \frac{di}{dt}$
- ▶ Frequency dependent impedance:  
 $Z = j\omega L$

# The Inductor

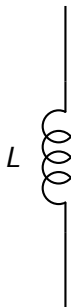

- ▶ I-V characteristics:  $V = L \frac{di}{dt}$
- ▶ Frequency dependent impedance:  
 $Z = j\omega L$
- ▶ No power dissipation (ideally)


# The Inductor

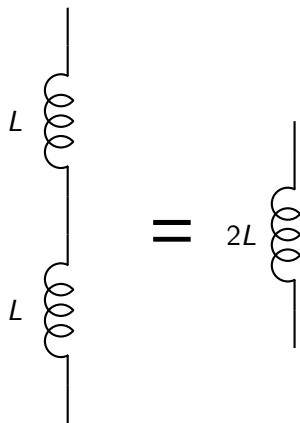

- ▶ I-V characteristics:  $V = L \frac{di}{dt}$
- ▶ Frequency dependent impedance:  $Z = j\omega L$
- ▶ No power dissipation (ideally)
- ▶ Add in series



# The Inductor

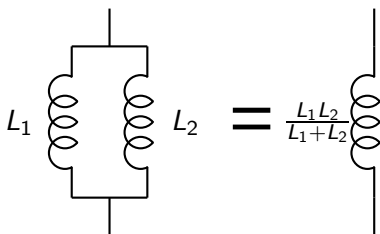

- ▶ I-V characteristics:  $V = L \frac{di}{dt}$
- ▶ Frequency dependent impedance:  $Z = j\omega L$
- ▶ No power dissipation (ideally)
- ▶ Add in series
- ▶ Inverse total equals inverse addition in parallel

# Overview

- ▶ Take advantage of frequency-dependence of components



# Overview

- ▶ Take advantage of frequency-dependence of components
- ▶ Filter out certain frequencies



# Overview

- ▶ Take advantage of frequency-dependence of components
- ▶ Filter out certain frequencies
- ▶ Each one characterized by a transfer function




# Overview

- ▶ Take advantage of frequency-dependence of components
- ▶ Filter out certain frequencies
- ▶ Each one characterized by a transfer function
- ▶ Many types (high-pass, low-pass, bandpass, band-reject)



## RC Low Pass Filter


- ▶ Uses a resistor and capacitor

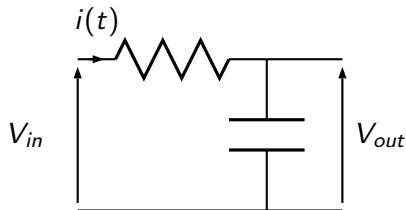
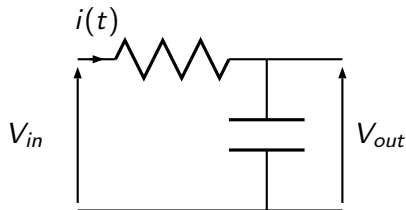
# RC Low Pass Filter

- ▶ Uses a resistor and capacitor
- ▶ Transfer function:

$$V_{out} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} V_{in}$$




## RC Low Pass Filter

- ▶ Uses a resistor and capacitor

- ▶ Transfer function:

$$V_{out} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} V_{in}$$

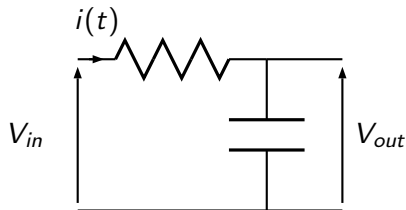
- ▶ Bandwidth: 0 to  $\omega_c = \frac{1}{RC}$





## RL Low Pass Filter


- ▶ Uses a resistor and inductor

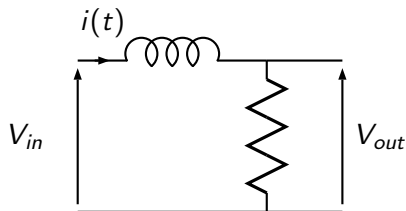
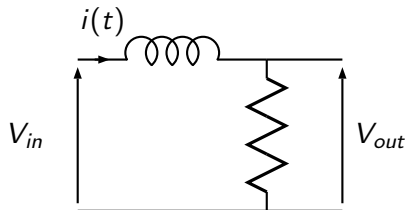
## RL Low Pass Filter

- ▶ Uses a resistor and inductor
- ▶ Transfer function:

$$V_{out} = \frac{\frac{R}{L}}{s + \frac{R}{L}} V_{in}$$




## RL Low Pass Filter

- ▶ Uses a resistor and inductor
- ▶ Transfer function:


$$V_{out} = \frac{\frac{R}{L}}{s + \frac{R}{L}} V_{in}$$

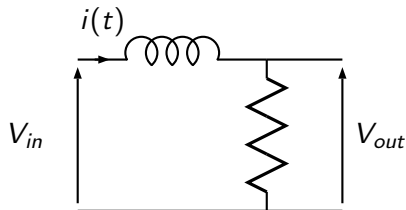- ▶ Bandwidth: 0 to  $\omega_c = \frac{R}{L}$



## RC High Pass Filter


- ▶ Uses a resistor and capacitor

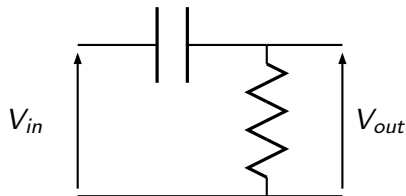
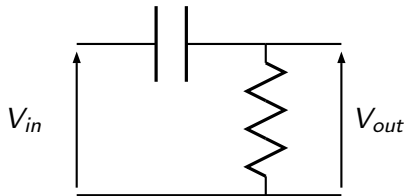
## RC High Pass Filter


- ▶ Uses a resistor and capacitor
- ▶ Transfer function:

$$V_{out} = \frac{s}{s + \frac{1}{RC}} V_{in}$$



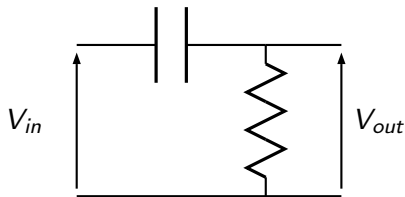
## RC High Pass Filter

- ▶ Uses a resistor and capacitor
- ▶ Transfer function:  
$$V_{out} = \frac{s}{s + \frac{1}{RC}} V_{in}$$
- ▶ Bandwidth:  $\omega_c = \frac{1}{RC}$  to  $\infty$



# RL High Pass Filter


- ▶ Uses a resistor and inductor

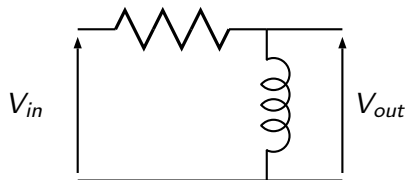
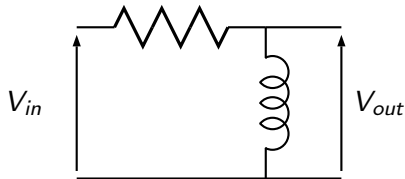
## RL High Pass Filter

- ▶ Uses a resistor and inductor
- ▶ Transfer function:


$$V_{out} = \frac{s}{s + \frac{R}{L}} V_{in}$$




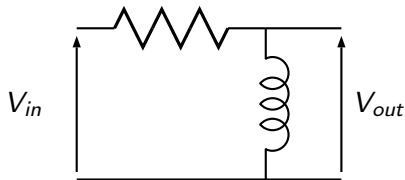
## RL High Pass Filter

- ▶ Uses a resistor and inductor
- ▶ Transfer function:  
$$V_{out} = \frac{s}{s + \frac{R}{L}} V_{in}$$
- ▶ Bandwidth:  $\omega_c = \frac{R}{L}$  to  $\infty$






## Series RLC Bandpass Filter

- ▶ Uses a resistor, inductor and capacitor

- ▶ Transfer function:
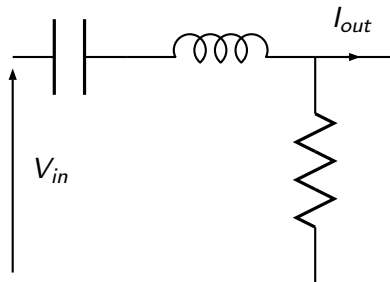
$$I_{out} = \frac{sC}{s^2 + s\frac{R}{L} + \frac{1}{LC}} V_{in}$$



## Series RLC Bandpass Filter

- ▶ Uses a resistor, inductor and capacitor


- ▶ Transfer function:

$$I_{out} = \frac{sC}{s^2 + s\frac{R}{L} + \frac{1}{LC}} V_{in}$$

- ▶ Bandwidth:


$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \text{ to}$$
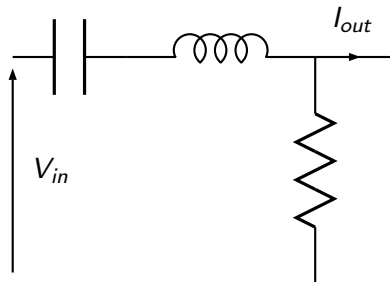
$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


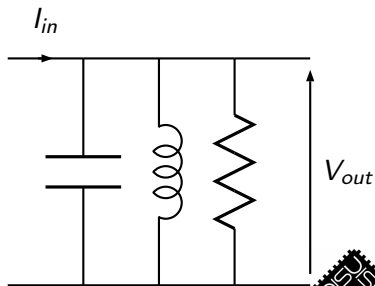
## Parallel RLC Bandpass Filter


- ▶ Uses a resistor, inductor and capacitor


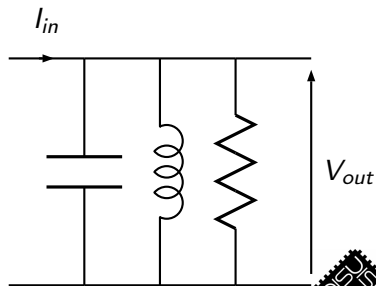
## Parallel RLC Bandpass Filter

- ▶ Uses a resistor, inductor and capacitor
- ▶ Transfer function:

$$V_{out} = \frac{s \frac{1}{C}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}} I_{in}$$



## Parallel RLC Bandpass Filter

- ▶ Uses a resistor, inductor and capacitor


- ▶ Transfer function:

$$V_{out} = \frac{s \frac{1}{C}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}} I_{in}$$

- ▶ Bandwidth:


$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$
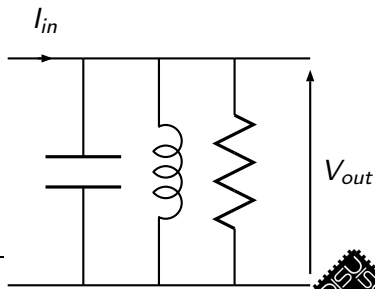
$$\text{to } \omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$


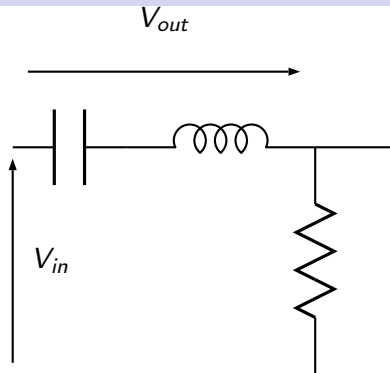
## RLC Bandreject Filter

- ▶ Uses a resistor, inductor and capacitor






## RLC Bandreject Filter

- ▶ Uses a resistor, inductor and capacitor

- ▶ Transfer function:
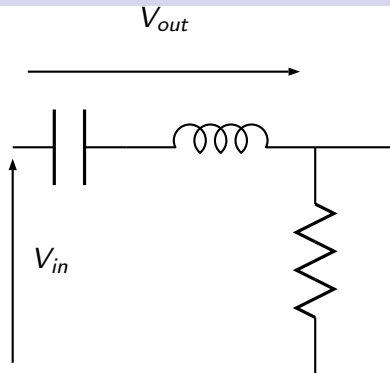
$$V_{out} = \frac{s^2 + \frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} V_{in}$$



## RLC Bandreject Filter

- ▶ Uses a resistor, inductor and capacitor


- ▶ Transfer function:

$$V_{out} = \frac{s^2 + \frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} V_{in}$$

- ▶ Rejection:

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \text{ to}$$
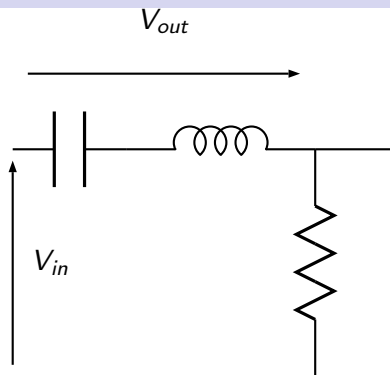
$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



# Overview

- ▶ Increase the magnitude of a certain input signal



# Overview

- ▶ Increase the magnitude of a certain input signal
- ▶ Very dependent on frequency




# Overview

- ▶ Increase the magnitude of a certain input signal
- ▶ Very dependent on frequency
- ▶ Several types, most popular is the operational amplifier (OpAmp)




# Overview

- ▶ Now implemented on ICs, cheap

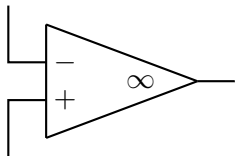

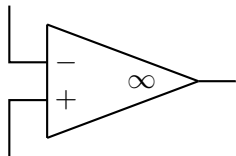
# Overview

- ▶ Now implemented on ICs, cheap
- ▶ Most widely used amplifier in electronics


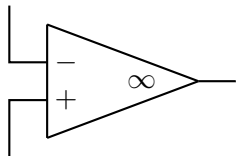
# Overview


- ▶ Now implemented on ICs, cheap
- ▶ Most widely used amplifier in electronics
- ▶ Differential inputs with high gain




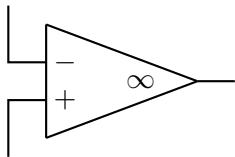
# Overview


- ▶ Now implemented on ICs, cheap
- ▶ Most widely used amplifier in electronics
- ▶ Differential inputs with high gain
- ▶ Gain usually maintained at constant value using negative feedback


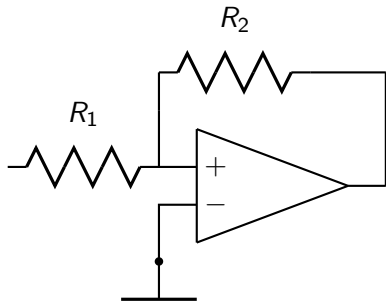
## Negative Feedback Configuration

- ▶ Amplifier Gain (ideal):

$$A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$




# Negative Feedback Configuration

- ▶ Amplifier Gain (ideal):

$$A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

- ▶ Amplifier Gain:
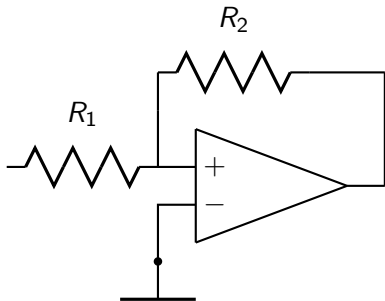
$$A_v = \frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \frac{s}{\omega_t/(1+R_2/R_1)}}$$



# Negative Feedback Configuration


- ▶ Amplifier Gain (ideal):

$$A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$


- ▶ Amplifier Gain:

$$A_v = \frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \frac{s}{\omega_t/(1+R_2/R_1)}}$$


- ▶ Usually has good frequency response

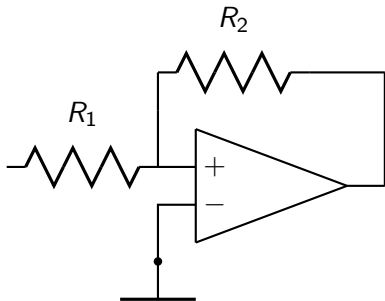

# Low Pass Filter

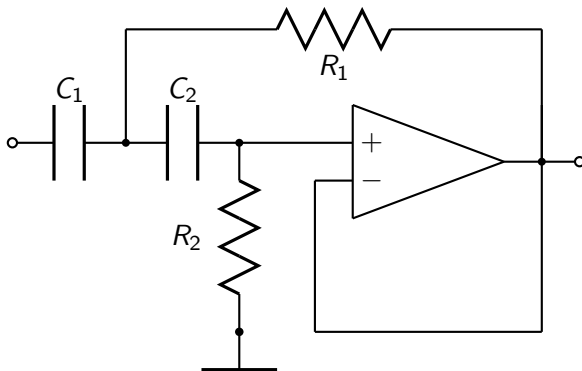

# High Pass Filter

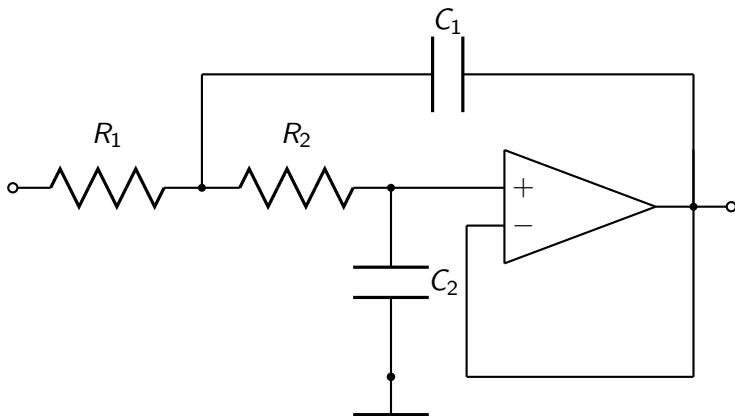

# Bandpass Filter

- ▶ Simplest: Combine high-pass and low-pass filter in series



# Bandpass Filter


- ▶ Simplest: Combine high-pass and low-pass filter in series
- ▶ Can also be done with single OpAmp






# Transistor Amplifiers

- ▶ Used in integrated circuits

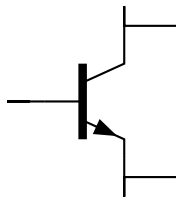

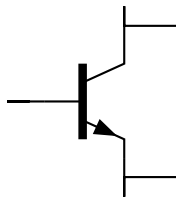
# Transistor Amplifiers

- ▶ Used in integrated circuits
- ▶ Will be our project's primary component


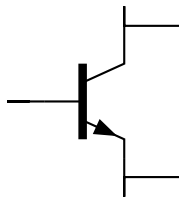
# Transistor Amplifiers

- ▶ Used in integrated circuits
- ▶ Will be our project's primary component
- ▶ Will be the subject of Tutorial 2



# Overview

- ▶ Very useful circuit simulation package



# Overview

- ▶ Very useful circuit simulation package
- ▶ Can simulate the characteristics of any circuit



# Overview

- ▶ Very useful circuit simulation package
- ▶ Can simulate the characteristics of any circuit
- ▶ Useful for ECE 100 labs, used in ECE 241 & 332



# Overview

- ▶ Very useful circuit simulation package
- ▶ Can simulate the characteristics of any circuit
- ▶ Useful for ECE 100 labs, used in ECE 241 & 332
- ▶ We will be using it to simulate the circuits discussed



# PSpice Syntax

- ▶ First line is always the title line





# PSpice Syntax

- ▶ First line is always the title line
- ▶ Syntax: NAME NODE\_A NODE\_B VALUE



# PSpice Syntax

- ▶ First line is always the title line
- ▶ Syntax: NAME NODE\_A NODE\_B VALUE
- ▶ Specify components according to their name



# PSpice Syntax

- ▶ First line is always the title line
- ▶ Syntax: NAME NODE\_A NODE\_B VALUE
- ▶ Specify components according to their name
  - ▶ Resistor: Rxx



# PSpice Syntax

- ▶ First line is always the title line
- ▶ Syntax: NAME NODE\_A NODE\_B VALUE
- ▶ Specify components according to their name
  - ▶ Resistor: Rxx
  - ▶ Capacitor: Cxx



# PSpice Syntax

- ▶ First line is always the title line
- ▶ Syntax: NAME NODE\_A NODE\_B VALUE
- ▶ Specify components according to their name
  - ▶ Resistor: Rxx
  - ▶ Capacitor: Cxx
  - ▶ Inductor: Lxx



## Sample Code - RC Low-Pass Filter

```
v.in 1 0 ac 1 pulse( -1 1 0 0 0 1m 2m )  
r1 1 2 10k  
c1 2 0 10n  
* analysis commands  
.ac dec 20 10 1meg  
.tran 700n 700u  
.probe  
.end
```

