
CSE477

VLSI Digital Circuits

Fall 2002

Lecture 25: Peripheral Memory Circuits

Mary Jane Irwin (www.cse.psu.edu/~mji)
www.cse.psu.edu/~cg477

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

Review: Read-Write Memories (RAMs)


❑ Static – SRAM

- data is stored as long as supply is applied
- large cells (6 fets/cell) – so fewer bits/chip
- fast – so used where speed is important (e.g., caches)
- differential outputs (output BL and !BL)
- use sense amps for performance
- compatible with CMOS technology

❑ Dynamic – DRAM

- periodic refresh required
- small cells (1 to 3 fets/cell) – so more bits/chip
- slower – so used for main memories
- single ended output (output BL only)
- need sense amps for correct operation
- not typically compatible with CMOS technology

Review: 4x4 SRAM Memory

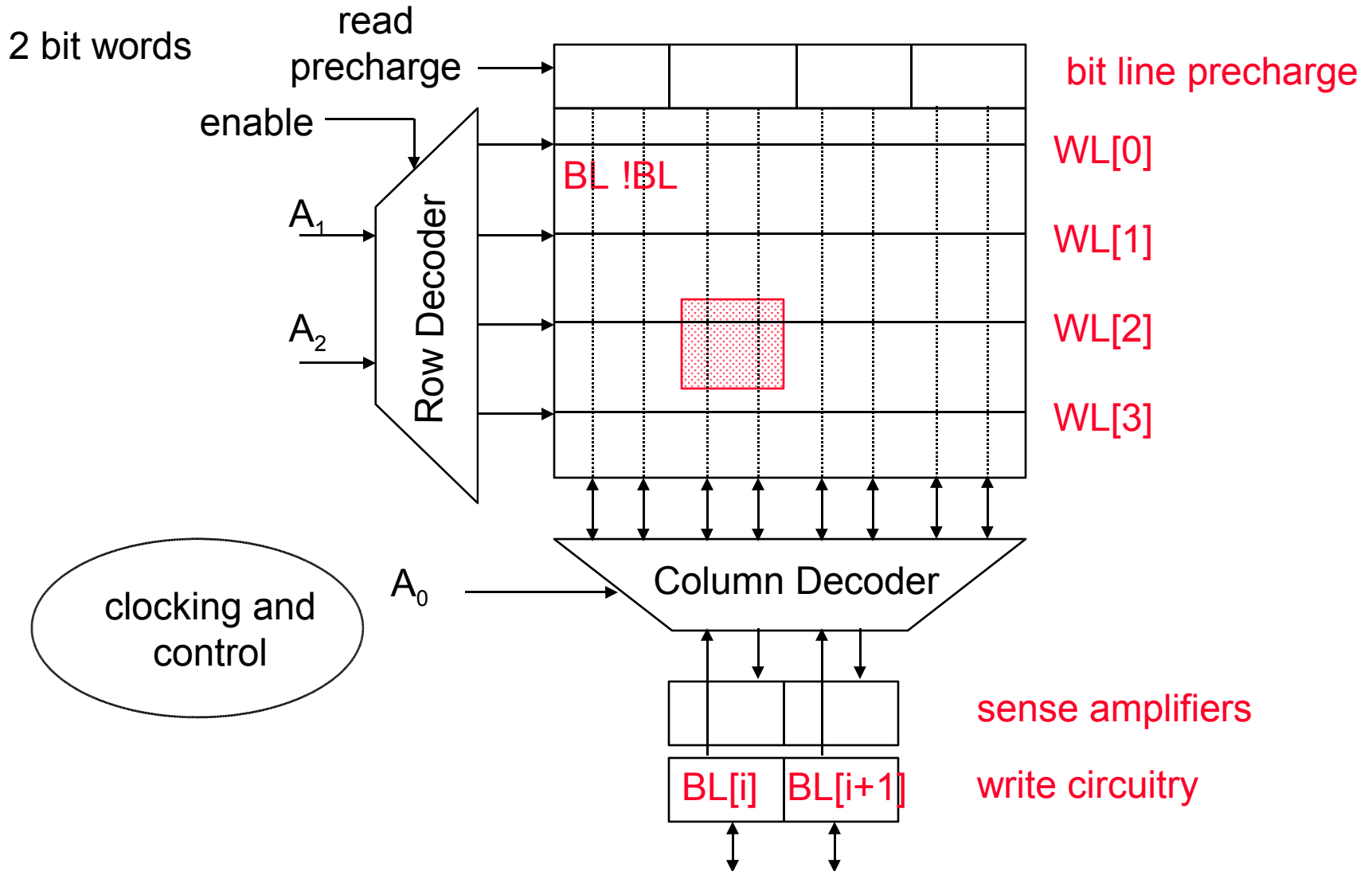

Peripheral Memory Circuitry

- ❑ Row and column decoders
- ❑ Sense amplifiers
- ❑ Read/write circuitry
- ❑ Timing and control

Row Decoders

- ❑ Collection of 2^M complex logic gates organized in a regular, dense fashion

- ❑ (N)AND decoder

$$WL(0) = !A_9!A_8!A_7!A_6!A_5!A_4!A_3!A_2!A_1!A_0$$

...

$$WL(511) = !A_9A_8A_7A_6A_5A_4A_3A_2A_1A_0$$


- ❑ NOR decoder

$$WL(0) = !(A_9+A_8+A_7+A_6+A_5+A_4+A_3+A_2+A_1+A_0)$$


...

$$WL(511) = !(A_9+!A_8+!A_7+!A_6+!A_5+!A_4+!A_3+!A_2+!A_1+!A_0)$$


Dynamic NOR Row Decoder

 


Dynamic NAND Row Decoder

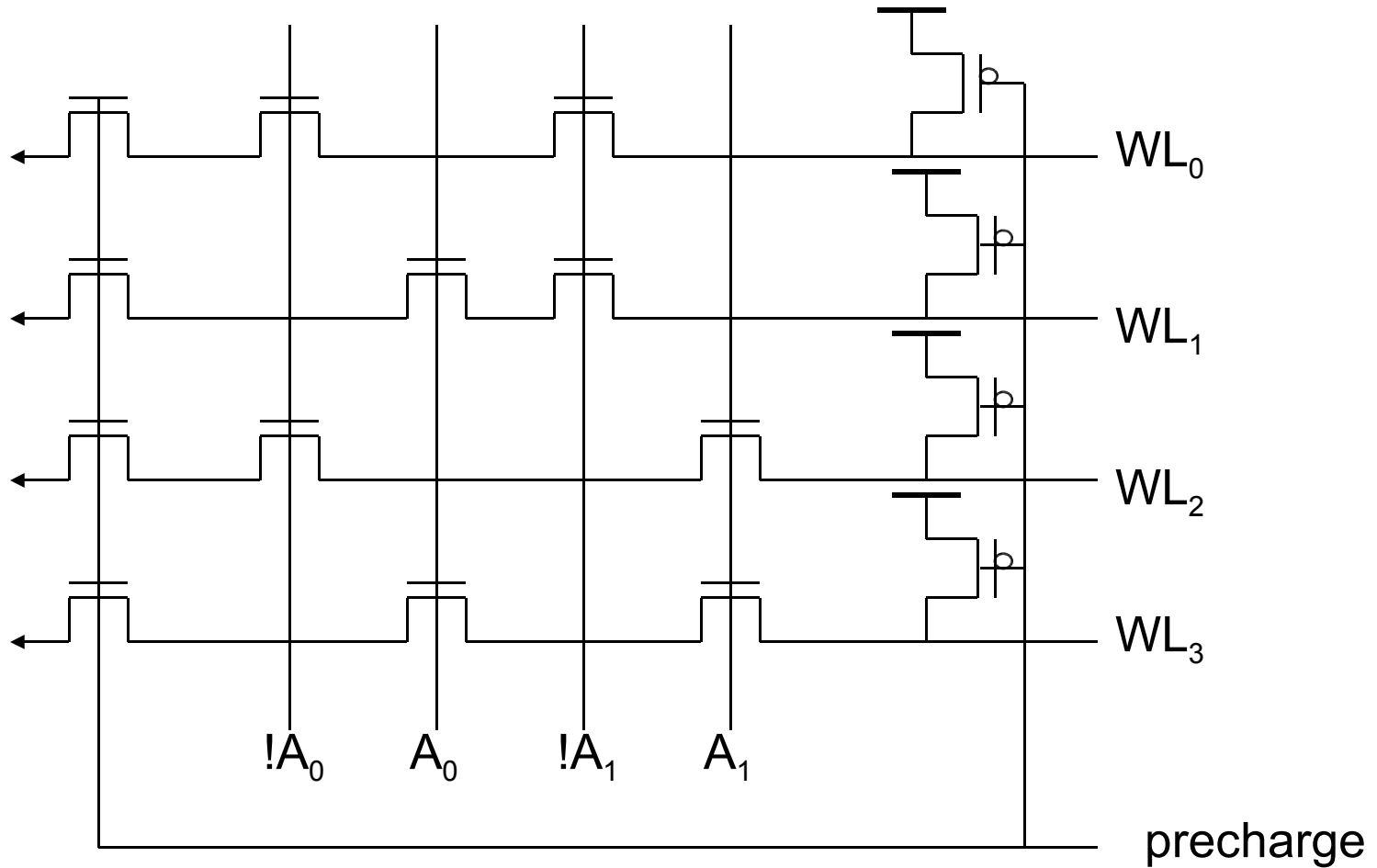

Split Row Decoder

 


Pass Transistor Based Column Decoder

 

- ❑ Advantage: speed since there is only one extra transistor in the signal path
- ❑ Disadvantage: large transistor count


Tree Based Column Decoder

 


- ❑ Advantage: number of transistors drastically reduced
- ❑ Disadvantage: delay increases quadratically with the number of sections (so prohibitive for large decoders)
 - fix with buffers, progressive sizing, combination of tree and pass transistor approaches

Bit Line Precharging

Static Pull-up Precharge

 

Clocked Precharge

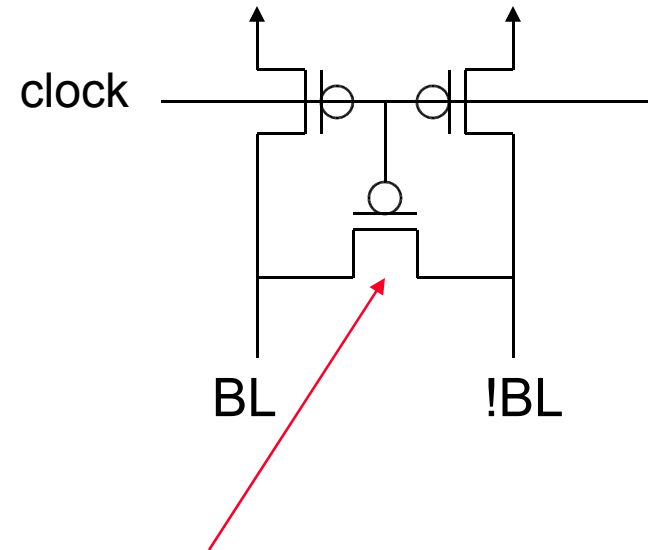

equalization transistor - speeds up equalization of the two bit lines by allowing the capacitance and pull-up device of the nondischarged bit line to assist in precharging the discharged line


Sense Amplifiers

$$t_p = (C * \Delta V) / I_{av}$$


Annotations for the equation:

- Red arrow pointing to C : large
- Red arrow pointing to ΔV : make ΔV as small as possible
- Red arrow pointing to I_{av} : small

 
- Use sense amplifiers (SA) to amplify the small swing on the bit lines to the full rail-to-rail swing needed at the output




Latch Based Sense Amplifier

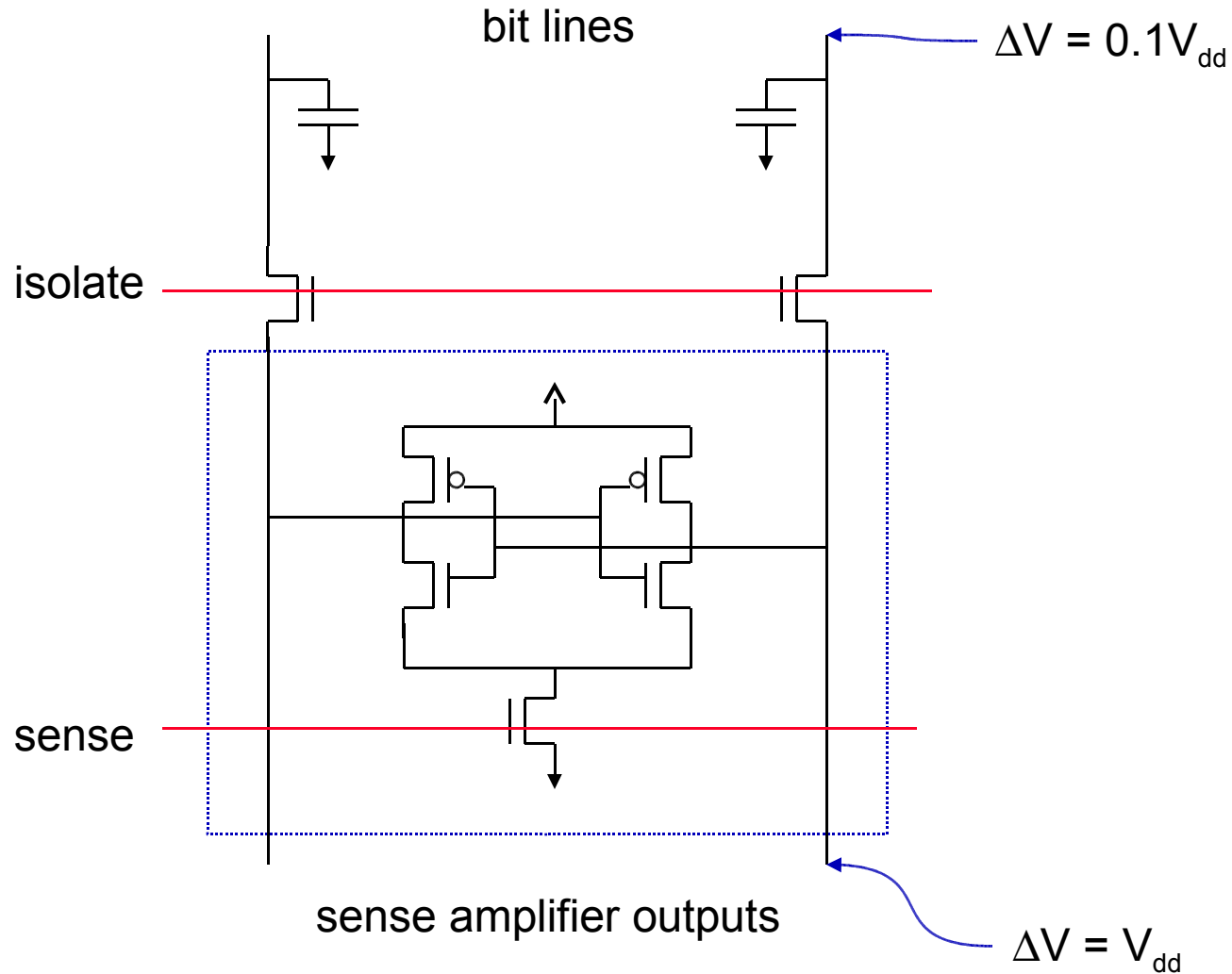

Alpha Differential Amplifier/Latch

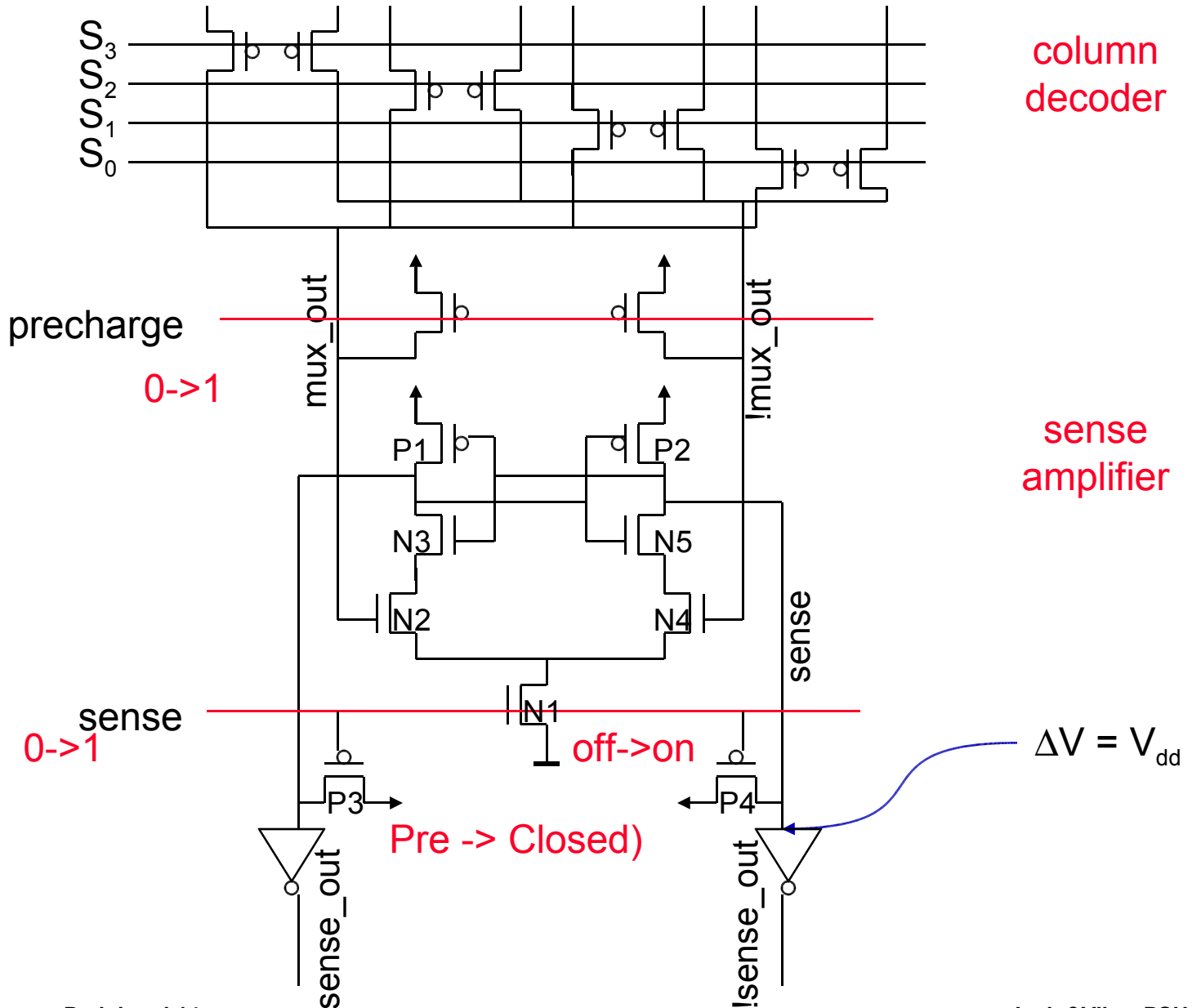

Read/Write Circuitry

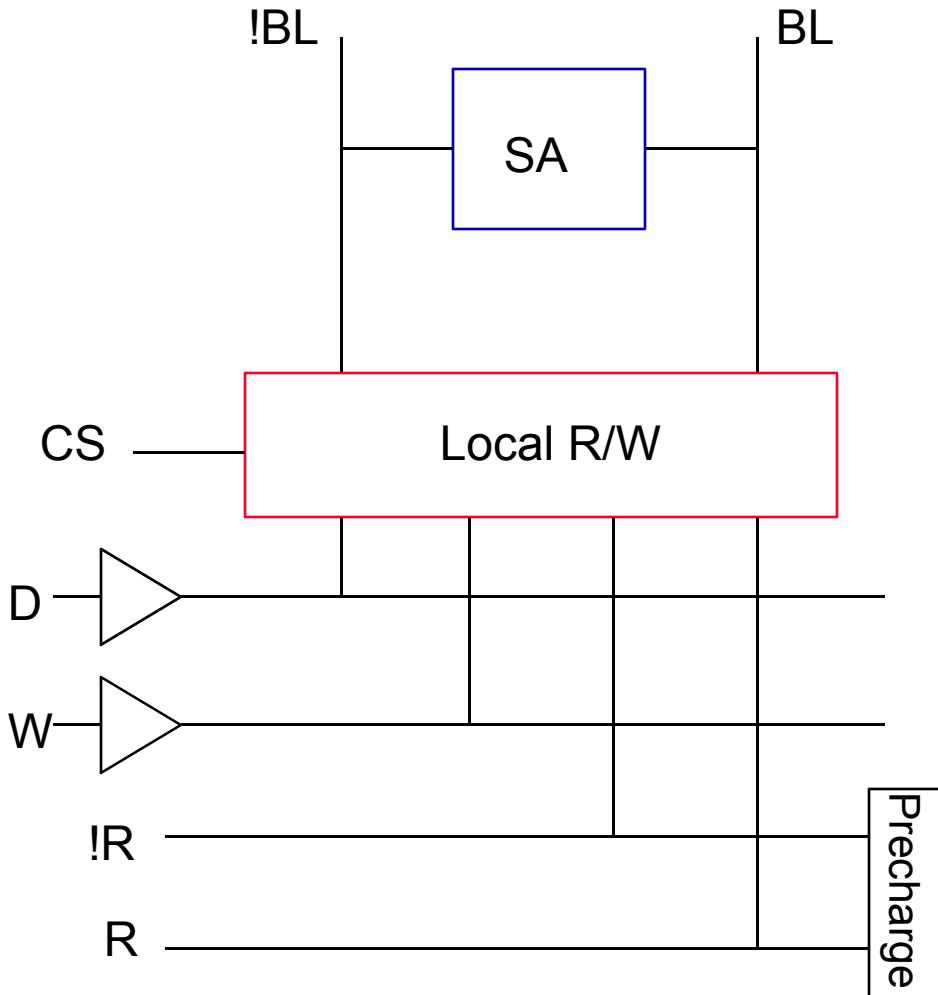


D: data (write) bus
 R: read bus
 W: write signal
 CS: column select
 (column decoder)

Local W (write):
 $BL = D, !BL = !D$
 enabled by W & CS


Local R (read):
 $R = BL, !R = !BL$
 enabled by !W & CS

Approaches to Memory Timing


SRAM Timing Self-Timed

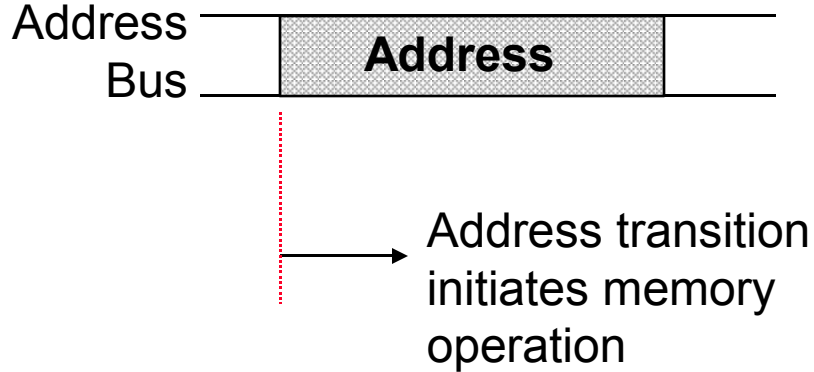


DRAM Timing Multiplexed Addressing

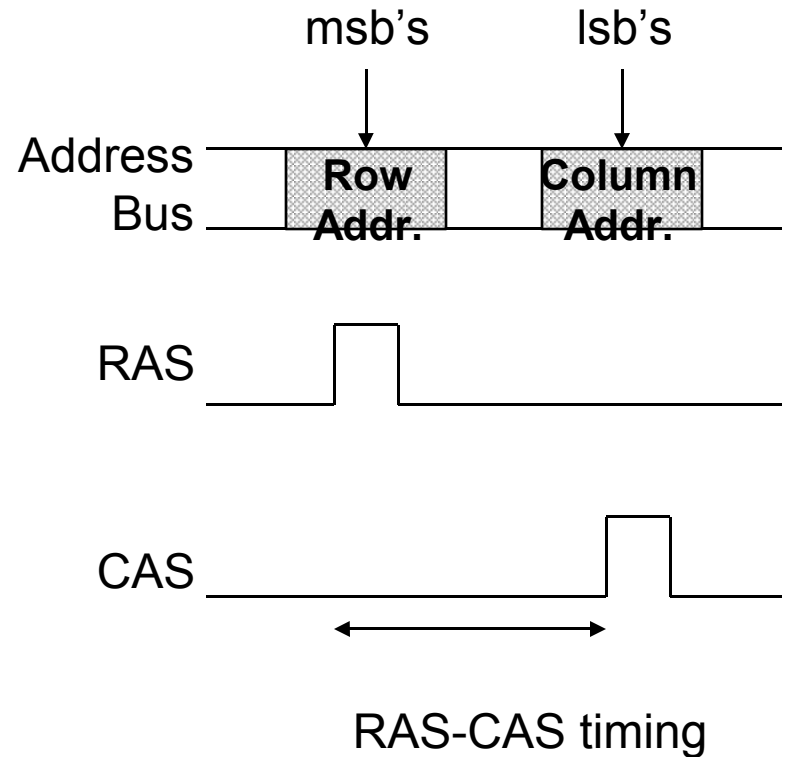

SRAM Address Transition Detection

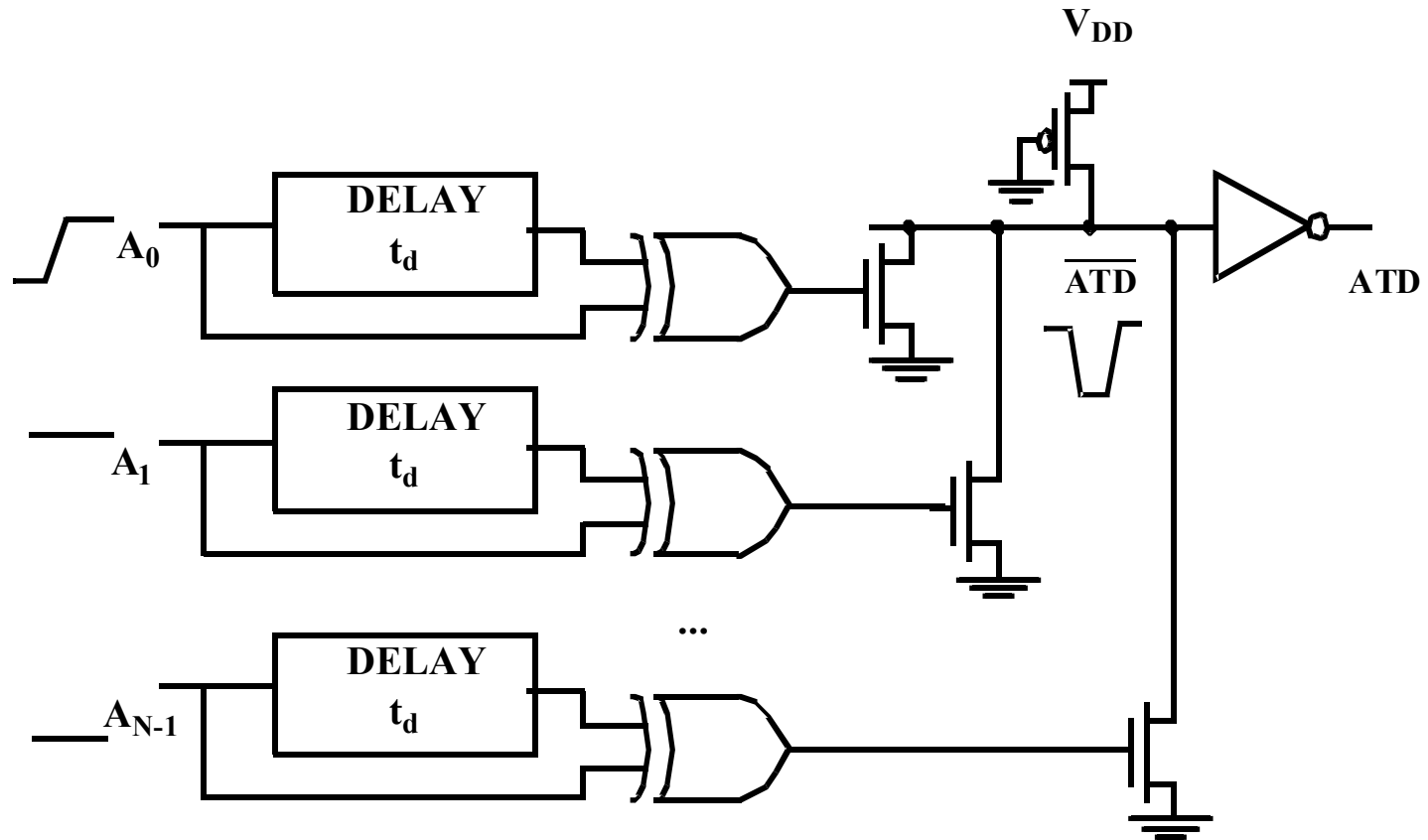


DRAM Timing

 

Review: A Typical Memory Hierarchy

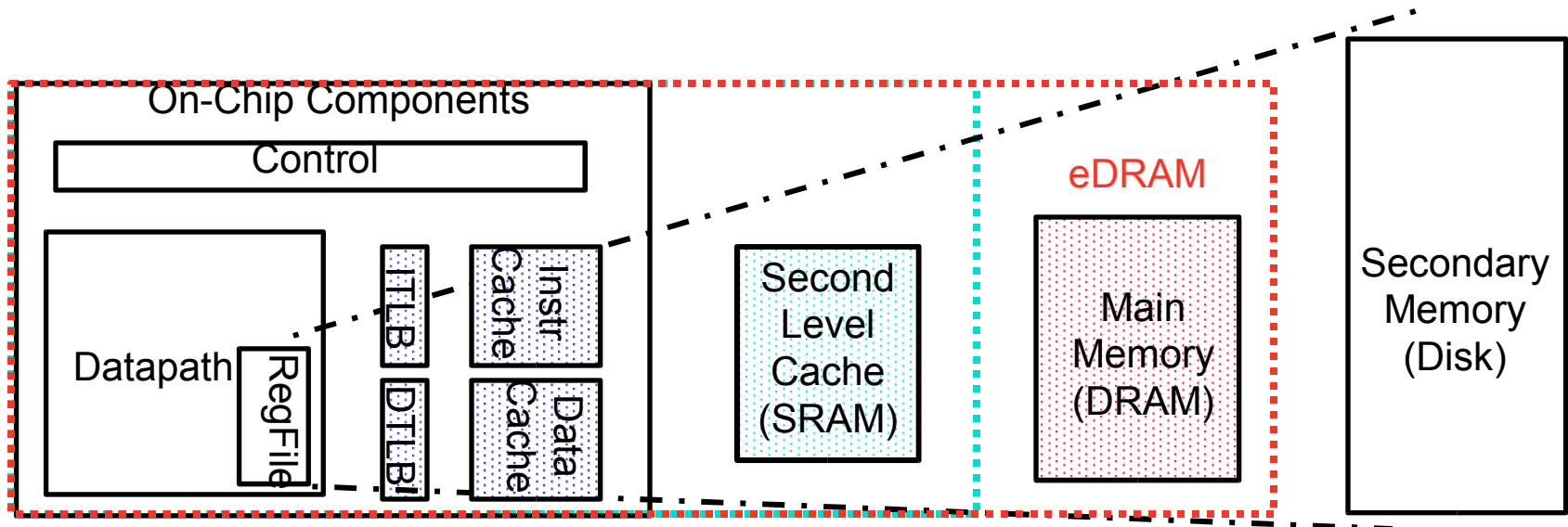
- By taking advantage of the principle of locality:
 - Present the user with as much memory as is available in the cheapest technology.
 - Provide access at the speed offered by the fastest technology.



Speed (ns):	.1's	1's	10's	100's	1,000's
Size (bytes):	100's	K's	10K's	M's	T's
Cost:	highest				lowest


Caches

 - Address issued by the data path has to be mapped (in hardware) into a cache address



- Cache block (aka line) – unit of read/write information in cache
- Cache mapping strategies
 - Direct mapped
 - A word can be in only one block in the cache, so only have to compare its tag against that block's tag
 - Block set associative
 - A word can be in two (or four or eight ...), so have to compare its tag against the tags of those two (or four or eight ...) cache blocks
 - Fully associative
 - A word can be in any block in the cache, so have to compare its tag against the tags of all of the blocks in the cache

Two-Way Block Set Associative Cache

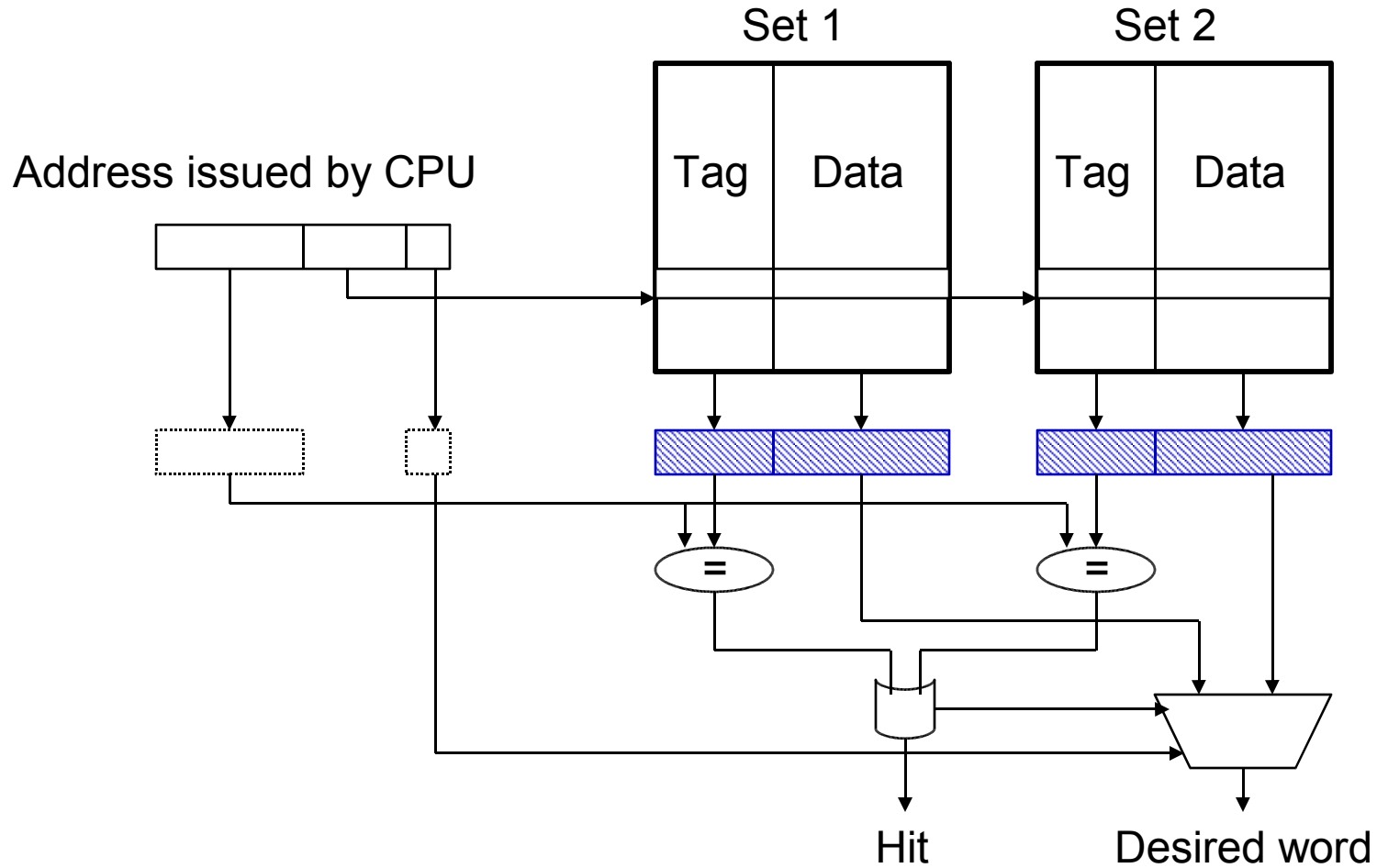


Translation Lookaside Buffers (TLBs)

- ❑ Small caches used to speed up address translation in processors with virtual memory
- ❑ All addresses have to be translated before cache access
- ❑ I\$ can be virtually indexed/virtually tagged


TLB Structure

 Address issued by CPU (page size = index bits + byte select bits)



Most TLBs are small (≤ 256 entries) and thus fully associative content addressable memories (CAMs)

CAM Design

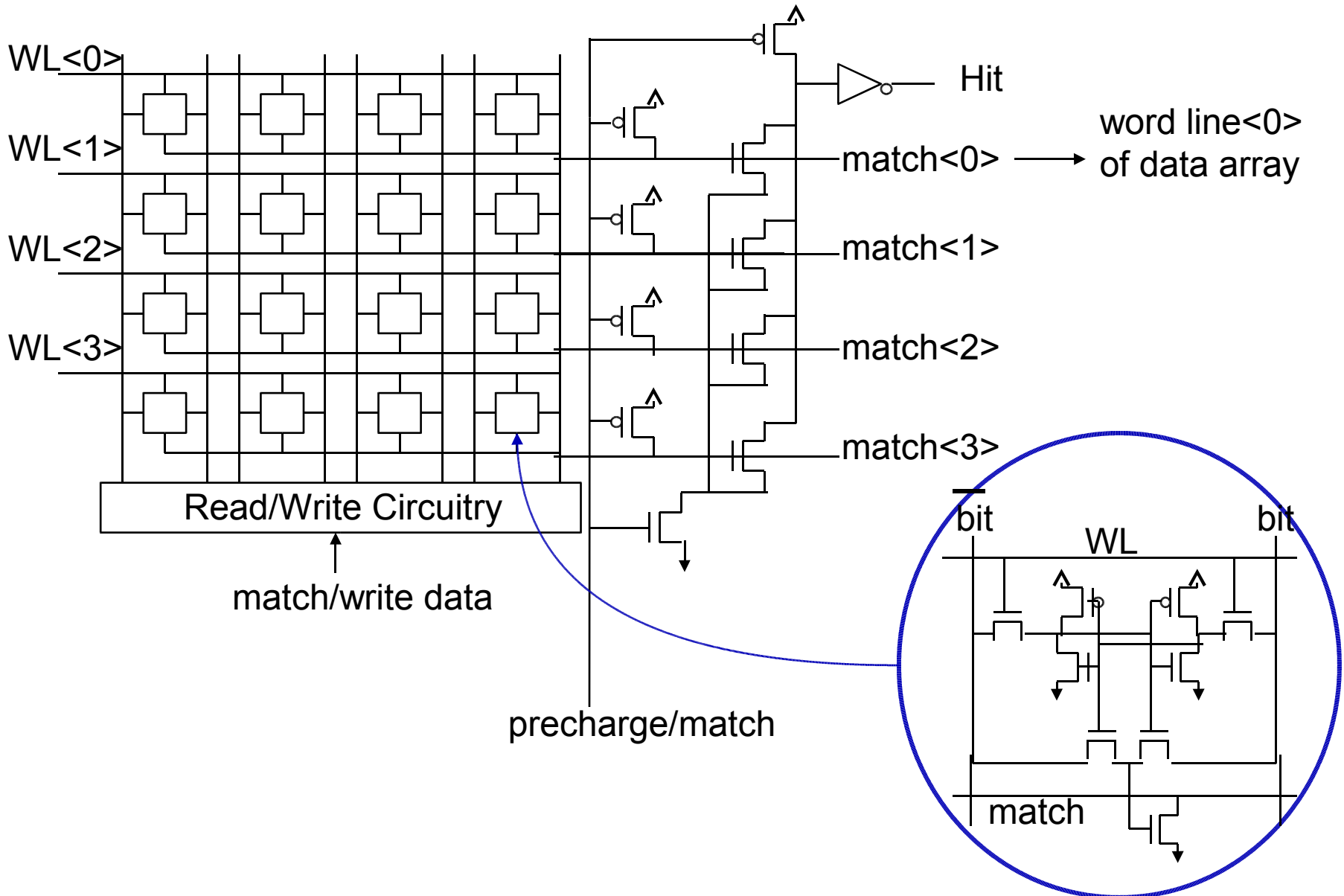

Reliability and Yield

- ❑ Semiconductor memories trade-off noise margin for density and performance

Thus, they are highly sensitive to noise (cross talk, supply noise)


- ❑ High density and large die size causes yield problems

$$\text{Yield} = 100 \frac{\text{\# of good chips/wafer}}{\text{\# of chips/wafer}}$$

$$Y = [(1 - e^{-AD})/(AD)]^2$$


- ❑ Increase yield using error correction and redundancy

Alpha Particles

 


1 particle ~ 1 million carriers

Yield

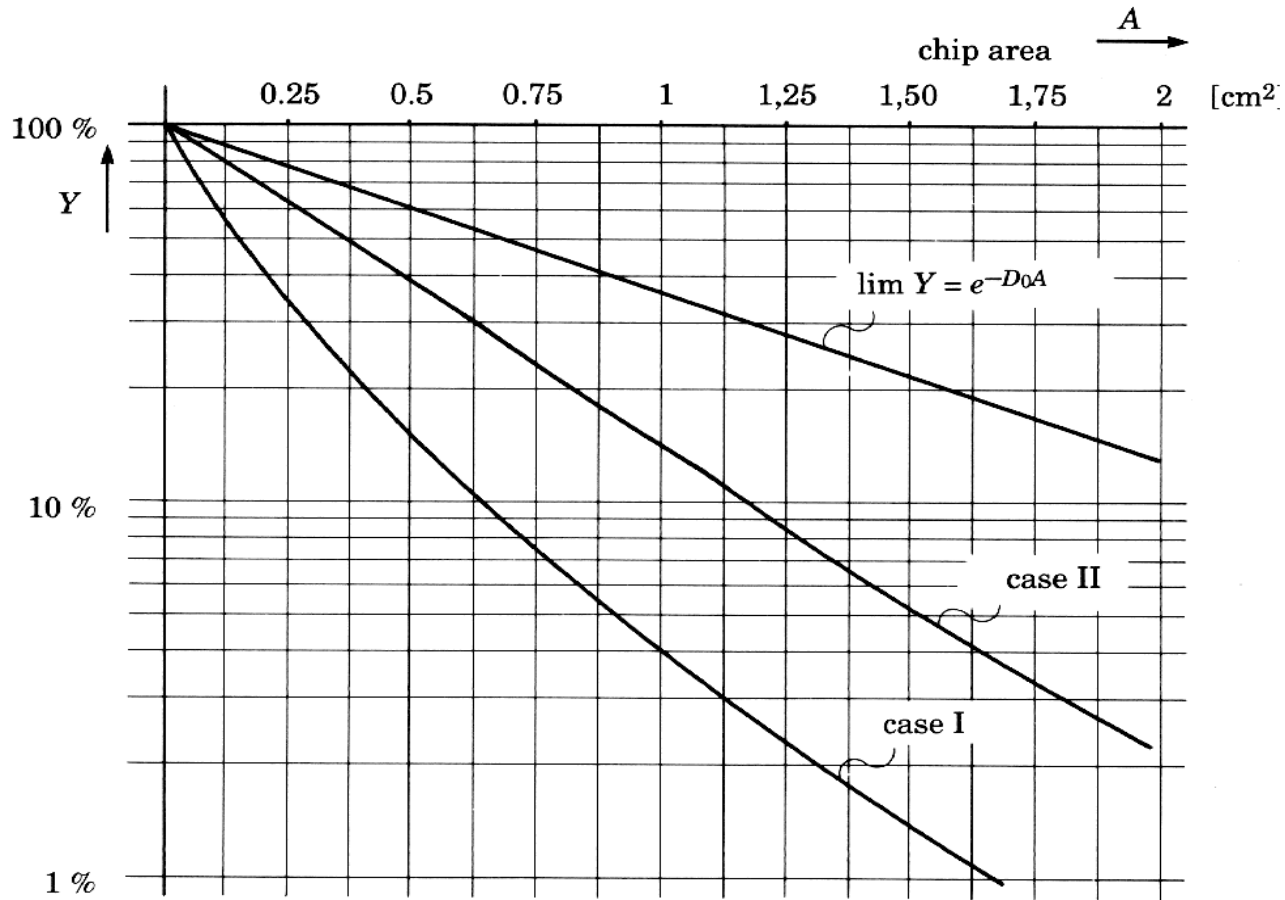


Yield curves at different stages of process maturity
(from [Veendrick92])

Redundancy in the Memory Structure

 

Redundancy and Error Correction

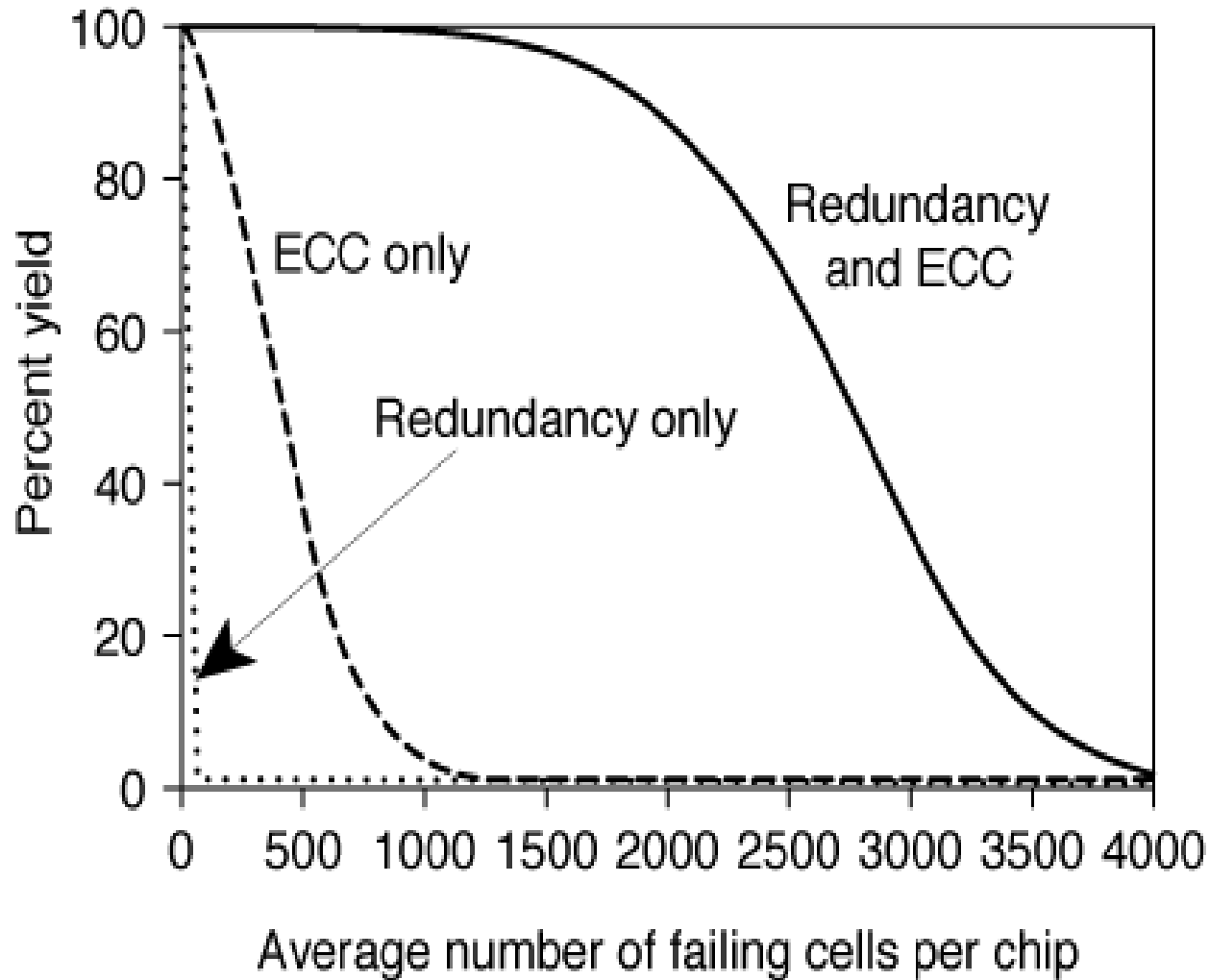

Next Lecture and Reminders

□ Next lecture

- System level interconnect
 - Reading assignment – Rabaey, et al, xx

□ Reminders

- Project final reports due December 5th
- Final grading negotiations/correction (except for the final exam) must be concluded by December 10th
- Final exam scheduled
 - Monday, December 16th from 10:10 to noon in 118 and 121 Thomas