 


Designing a Simple FPGA-Optimized RISC CPU and System-on-a-Chip

Jan Gray, Gray Research LLC

`jsgray@acm.org`

`www.fpgacpu.org`



`lw r12,4(r3)`

About this talk

■ Themes

- FPGA soft CPU cores can be quite compact
- For best results, design with the FPGA in mind
- CPU design is not rocket science

■ Approach – let's design one

- Study one implementation *in detail*
- Highlight FPGA optimizations


Introduction

- FPGAs: not just glue logic
 - \$10-\$20 for 100K gates ('2S100)
 - CPU <10% of chip => cost effective SoC
 - Skip the discrete CPU, skip the ASIC, ship the FPGA
- Advantages
 - Integration, TTM, low NREs, field upgrades
 - Custom instructions, function units, coprocessors
 - Own your IP, control your destiny (end of life)
 - Skip cosimulation?
- Or trade software for complex blocks of logic


Outline

- Introduction
- **FPGA Architecture**
- Design of CPU and SoC
 - RISC CPU core
 - System-on-a-chip and peripherals
- Results, comparisons
- Software tools
- Conclusions

Xilinx Virtex Architecture

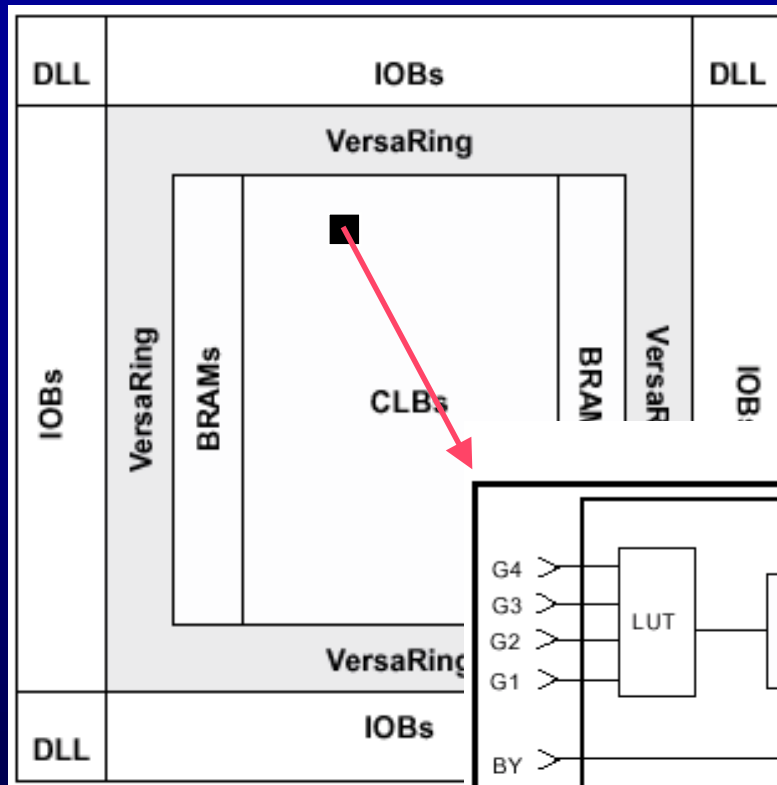

Source: Xilinx

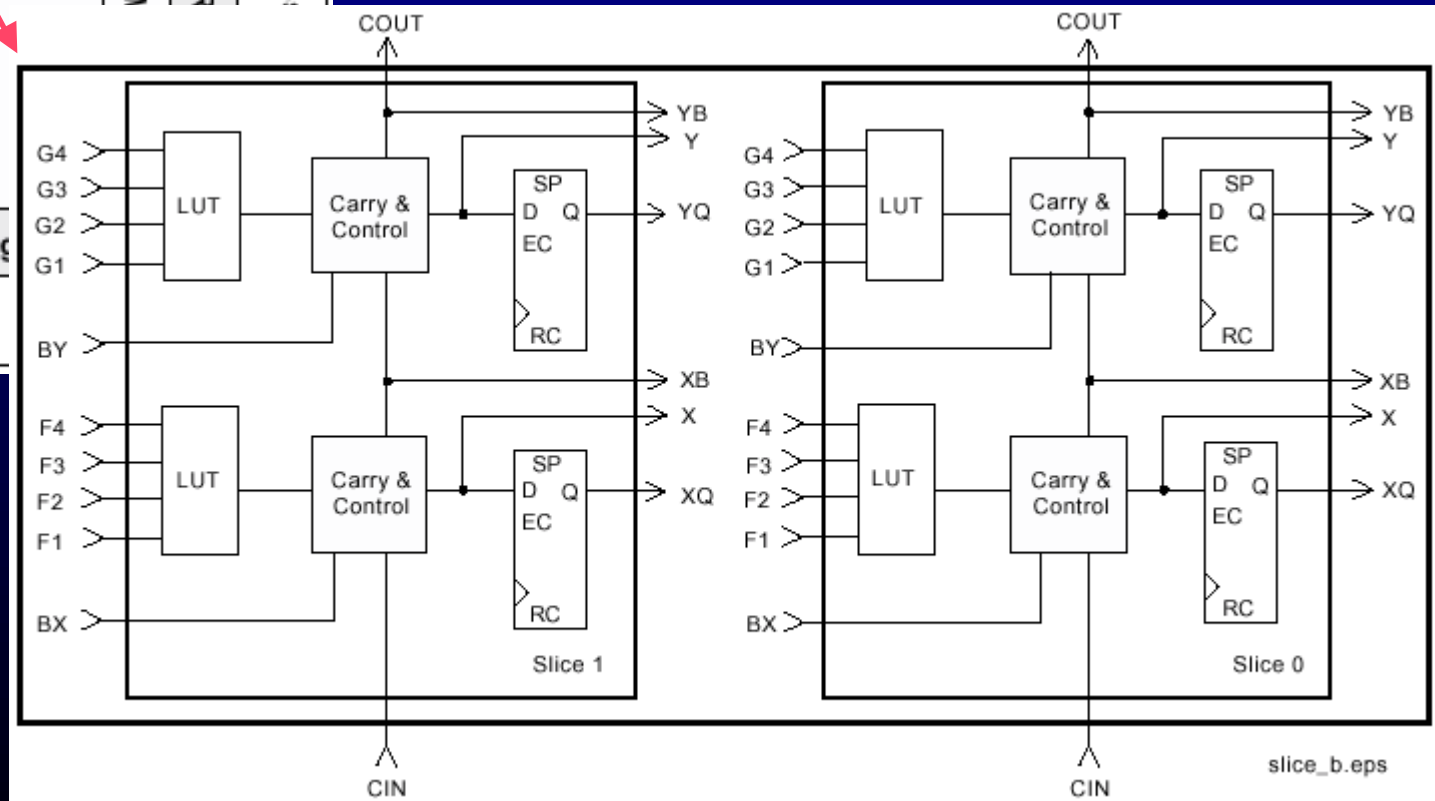

Xilinx XC2S50-5TQ144 FPGA

- 2.5V 144-pin quad flat pack, 92 I/Os
- 16R x 24C array of config logic blocks (CLBs)
 - Each with 2 slices each with 2 logic cells
 - Each cell with a 4-input lookup table, flip-flop
 - Two LUTs = one 16x1 dual port RAM
- 8 block RAMs
 - Dual ported, 4 Kb (256 x 16b), *0 cycle latency*
- Programmable interconnect
 - Hierarchical, plus buses via TBUFs (3-state buffers)

Outline

- Introduction
- FPGA Architecture
- Design of CPU and SoC
 - RISC CPU core
 - System-on-a-chip and peripherals
- Results, comparisons
- Software tools
- Conclusions

Designing a *Simple* CPU and System

- No longer rocket science; thanks to
 - FPGAs: abstraction of a perfect digital world
 - Tools: design implementation; retargetable compilers
- Simple is beautiful
 - Simpler is smaller; smaller is ...
 - Cheaper – less area
 - Faster – shorter ‘wires’, easier to fix speed problems
 - Power frugal – less wires to discharge each cycle
 - Simpler is easier to test

Example System: RISC MCU SoC

- GR0040 – a simple CPU core
- GR0041 – GR0040 plus interrupt handling
- SOC – a simple system-on-a-chip
 - GR0041 CPU
 - 1 KB block RAM instruction and data memory
 - Glueless on-chip bus
 - Peripherals: parallel port, counter/timer
- See paper for annotated Verilog source code

GR0040 CPU Core

- An simple RISC core for integer C code
 - One instruction per cycle, non-pipelined
 - Compact => inexpensive
 - 200 lines of Verilog
 - FPGA optimized: ISA, implementation
- 16-bits, 16 registers
 - Scales to 32-bit registers
- Key Ideas
 - Use 0-cycle BRAM for instruction store
 - Use a dual-port LUT RAM bank for register file

GR0040 Instruction Set Architecture


Format	15	12	11	8	7	4	3	0
rr	op	rd	rs	fn				
ri	op	rd	fn	imm				
rri	op	rd	rs	imm				
i12	op	imm12						
br	op	cond	disp8					

Hex	Fmt	Assembler	Semantics
0d <i>si</i>	rri	jal rd,imm(rs)	rd = pc, pc = imm+rs;
1d <i>si</i>	i12	addi rd,rs,imm	rd = imm+rs;
2d <i>s*</i>	rr	{add sub adc sbc and or xor andn cmp srl sra } rd,rs	rd = rd <i>fn</i> rs;
3d <i>*I</i>	ri	{- rsubi adci rsbci andi ori xori andni rcmpi } rd,imm	rd = imm <i>fn</i> rd;
4d <i>si</i>	rri	lw rd,imm(rs)	rd = *(int*)(imm+rs);
5d <i>si</i>	rri	lb rd,imm(rs)	rd = *(byte*)(imm+rs);
6d <i>si</i>	rri	sw rd,imm(rs)	*(int*)(imm+rs) = rd;
7d <i>si</i>	rri	sb rd,imm(rs)	*(byte*)(imm+rs) = rd;
8i <i>ii</i>	i12	imm imm12	imm'next _{15:4} = imm12;
9d <i>dd</i>	br	{br brn beq bne bc bnc bv bnv blt bge ble bgt bltu bgeu bleu bgtu} label	if (<i>cond</i>) pc += 2*disp8;


GR0040 Synthesized Instructions

Assembly	Maps to
nop	xor r0,r0
mov rd,rs	addi rd,rs,0
subi rd,rs,imm	addi rd,rs,-imm
neg rd	rsubi rd,0
com rd	xori rd,-1
sll rd	add rd,rd
lea rd,imm(rs)	addi rd,rs,imm
j ea	imm ea _{15:4} jal r1,ea _{3:0}
call fn	imm fn _{15:4} jal r15,fn _{3:0}
ret	jal r1,2(r15)
lbs rd,imm(ra) <i>(load-byte, sign-extending)</i>	lb rd,imm(ra) lea r1,0x80 xor rd,r1 sub rd,r1

GR0040 Core Symbol

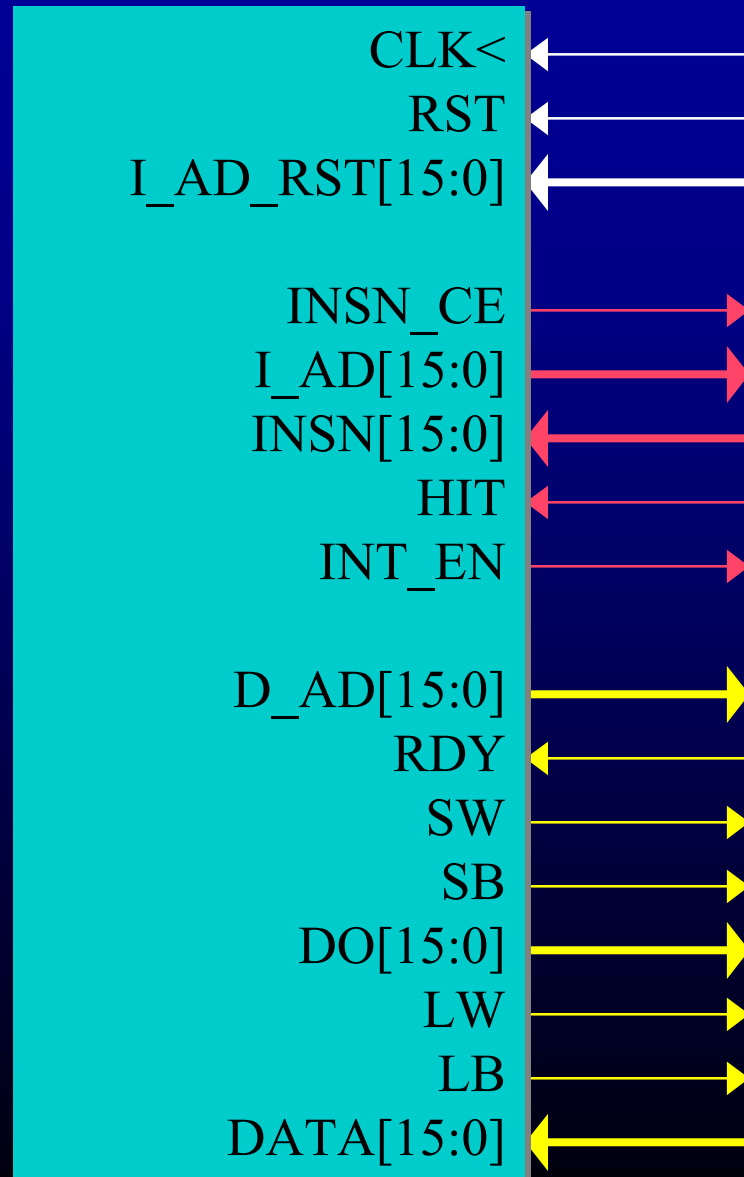

GR0040 Logical Block Diagram

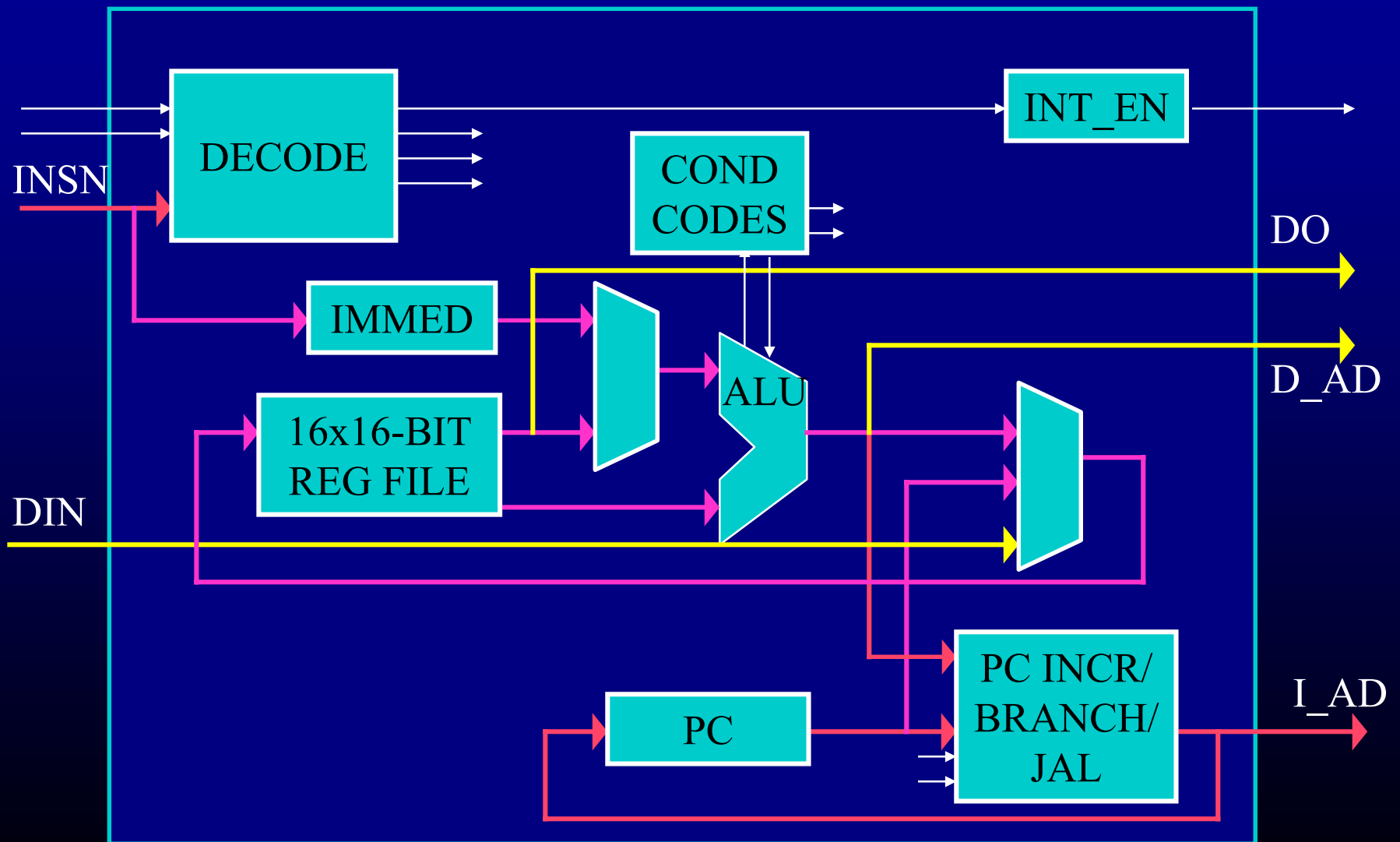

GR0040 Implementation Outline

- Interface
- Instruction decoding
- Register file and PC
- Immediate literals
- Operand selection
- ALU
 - Adder/subtractor
 - Condition codes
 - Logic unit, shifts
- Result multiplexer
- Jumps and branches
 - Branch decoding
 - Branch logic
 - Next instruction address
- Data load/store controls
- Interrupt enable

GR0040 Interface (1)

■ Module

```
module gr0040(  
    clk, rst, i_ad_rst,  
    insn_ce, i_ad, insn, hit, int_en,  
    d_ad, rdy, sw, sb, do, lw, lb, data);
```

```
    input  clk;           // clock  
    input  rst;          // reset (sync)  
    input  [`AN:0] i_ad_rst; // reset vector
```


GR0040 Interface (2)

■ Instruction Port

```
output insn_ce;           // insn clock enable  
output [`AN:0] i_ad;    // next insn address  
input  [`IN:0] insn;    // current insn  
input  hit;             // insn is valid  
output int_en;         // OK to intr. now
```

■ Data Port

```
output [`AN:0] d_ad;    // load/store addr  
input  rdy;            // memory ready  
output sw, sb;         // executing sw (sb)  
output [`N:0] do;      // data to store  
output lw, lb;         // executing lw (lb)  
inout  [`N:0] data;    // results, load data
```

Instruction Field Cracking

// instruction decoding

```
wire [3:0] op    = insn[15:12];
```

```
wire [3:0] rd    = insn[11:8];
```

```
wire [3:0] rs    = insn[7:4];
```

```
wire [3:0] fn    = `RI? insn[7:4] : insn[3:0];
```

```
wire [1:0] logop = fn[1:0];
```

```
wire [3:0] imm   = insn[3:0];
```

```
wire [11:0] i12  = insn[11:0];
```

```
wire [3:0] cond  = insn[11:8];
```

```
wire [7:0] disp  = insn[7:0];
```

Opcode Decoding

```
// opcode decoding
`define JAL      (op==0)
`define ADDI    (op==1)
`define RR      (op==2)
`define RI      (op==3)
`define LW      (op==4)
`define LB      (op==5)
`define SW      (op==6)
`define SB      (op==7)
`define IMM     (op==8)
`define BX      (op==9)
`define ALU     (`RR | `RI)
```

Function Field Decoding

```
// fn decoding
`define ADD      (fn==0)
`define SUB      (fn==1)
`define ADC      (fn==2)
`define SBC      (fn==3)
`define AND      (fn==4)
`define OR       (fn==5)
`define XOR      (fn==6)
`define ANDN     (fn==7)
`define CMP      (fn==8)
`define SRL      (fn==9)
`define SRA      (fn=='hA)
`define SUM      (`ADD | `SUB | `ADC | `SBC)
`define LOG      (`AND | `OR | `XOR | `ANDN)
`define SR       (`SRL | `SRA)
```

Register File Design

- Key issue
- FPGA RAM primitives
 - Single port or dual port LUT RAM
 - Single/dual port block RAM
- Getting to 2R-1W per cycle
 - Time multiplex access
 - Replicas
- GR0040: dual port LUT RAM
 - Write and read via write-port, read via read-port
 - Perfect fit for $rd = rd \text{ op } rs;$

Register File and Program Counter

```
// register file and program counter
wire valid_insn_ce = hit & insn_ce;
wire rf_we = valid_insn_ce & ~rst &
             ((`ALU&~`CMP)|`ADDI|`LB|`LW|`JAL);
wire [`N:0] dreg, sreg; // d, s registers

ram16x16d regfile(.clk(clk), .we(rf_we),
                 .wr_addr(rd), .addr(`RI ? rd : rs),
                 .d(data), .wr_o(dreg), .o(sreg));

reg [`AN:0] pc; // program counter
```

12-bit Immediate Prefix

■ Example

➤ `imm 0x123`
`addi r2,r1,4 ; r2 = r1 + 0x1234`

■ Verilog

```
// immediate prefix  
reg imm_pre; // immediate prefix  
reg [11:0] i12_pre; // imm prefix value
```

```
always @(posedge clk)  
  if (rst)  
    imm_pre <= 0;  
  else if (valid_insn_ce)  
    imm_pre <= `IMM;  
always @(posedge clk)  
  if (valid_insn_ce)  
    i12_pre <= i12;
```

16-bit Immediate Operand

- 4-bits sign-extended, zero-extended, scaled x2, 12-bit prefix || 4-bit immediate

```
// immediate operand
wire word_off = `LW|`SW|`JAL;
wire sxi = (`ADDI|`ALU) & imm[3];
wire [10:0] sxi11 = {11{sxi}};
wire i_4 = sxi | (word_off&imm[0]);
wire i_0 = ~word_off&imm[0];

wire [`N:0] imm16 = imm_pre ? {i12_pre,imm}
                        : {sxi11,i_4,imm[3:1],i_0};
```


Operand Selection

■ Examples

```
add  r2,r1      // a=r2 b=r1
addi r4,r3,4    // a=4  b=r3
andi r5,3       // a=3  b=r5
lw   r6,2(sp)  // a=2  b=r14
```

■ Verilog

```
// operand selection
```

```
wire [`N:0] a = `RR ? dreg : imm16;
```

```
wire [`N:0] b = sreg;
```

■ Possible tech mapping opt for 50% area savings

➤ $o = s1 ? (s2?a:b) : s2$; (one 4-LUT per bit)

ALU: Adder/Subtractor

```
// adder/subtractor
wire [`N:0] sum;
wire add = ~(`ALU&(`SUB|`SBC|`CMP));
reg c; // carry-in if adc/sbc
wire ci = add ? c : ~c;
wire c_w, x;

// assign {co,sum,x}= add ? {a,ci}+{b,1'b1}
//                               : {a,ci}-{b,1'b1};

addsub adder(.add(add), .ci(ci), .a(a),
             .b(b), .sum(sum), .x(x), .co(c_w));
```

Oops!

- Synplicity missed resource sharing opportunity
 - Got mux, add, sub – 200% larger than necessary

- Fix

```
module addsub(add, ci, a, b, sum, x, co);  
    input  add, ci;  
    input  [15:0] a, b;  
    output [15:0] sum;  
    output x, co;  
    assign {co,sum,x} = add ? {a,ci}+{b,1'b1}  
                        : {a,ci}-{b,1'b1};  
  
endmodule
```

- Moral: check synthesis results!

Condition Codes

```
// condition codes
wire z = sum == 0;           // zero
wire n = sum[`N];          // negative
wire co = add ? c_w : ~c_w; // carry-out
wire v = c_w^sum[`N]^a[`N]^b[`N]; // overflow

reg ccz, ccn, ccc, ccv; // CC register
always @(posedge clk)
  if (rst)
    {ccz, ccn, ccc, ccv} <= 0;
  else if (valid_insn_ce)
    {ccz, ccn, ccc, ccv} <= {z, n, co, v};
```

Add/Sub with Carry

```
// add/subtract-with-carry state  
always @(posedge clk)  
    if (rst)  
        c <= 0;  
    else if (valid_insn_ce)  
        c <= co & (`ALU&(`ADC|`SBC));
```

ALU: Logic Unit and Shift Right

```
// logic unit
```

```
reg [`N:0] log;
```

```
always @(a or b or logop)
```

```
    case (logop)
```

```
    0: log = a & b;
```

```
    1: log = a | b;
```

```
    2: log = a ^ b;
```

```
    3: log = a & ~b;
```

```
    endcase
```

```
// shift right
```

```
wire [`N:0] sr = {(`SRA?b[`N]:0), b[`N:1]};
```

- Delete or and andn, save >50%

GR0040 Implementation Outline

- Interface
- Instruction decoding
- Register file and PC
- Immediate literals
- Operand selection
- ALU
 - Adder/subtractor
 - Condition codes
 - Logic unit, shifts
- Result multiplexer
- Jumps and branches
 - Branch decoding
 - Branch logic
 - Next instruction address
- Data load/store controls
- Interrupt enable

Result Multiplexer

```
// result mux
```

```
wire sum_en = (`ALU&`SUM) | `ADDI;
```

```
assign data = sum_en      ? sum : 16'bz;
```

```
assign data = (`ALU&`LOG) ? log : 16'bz;
```

```
assign data = (`ALU&`SR)  ? sr  : 16'bz;
```

```
assign data = `JAL        ? pc   : 16'bz;
```

- FPGA optimization of wide n-input multiplexer
 - Use *free* TBUFs instead of logic muxes
 - Saves tons of logic and interconnect
 - *Impractical on TBUF-poor Virtex-II*

Brief Digression on Customization

- Single cycle – add new function unit

```
wire [`N:0] pop = b[0] + b[1] + ... + b[`N];  
`define POP (fn == 'hB)  
assign data = (`ALU&`POP) ? pop : 16'bz;
```

- Multicycle – add memory mapped coprocessor

Conditional Branch Decoding

// conditional branch decoding

```
`define BR      0
`define BEQ     2
`define BC      4
`define BV      6
`define BLT     8
`define BLE     'hA
`define BLTU    'hC
`define BLEU    'hE
```

Conditional Branch Decision

```
// conditional branches
reg br, t;
always @(hit or cond or op or
        ccz or ccn or ccc or ccv) begin
    case (cond&4'b1110)
        `BR:    t = 1;
        `BEQ:   t = ccz;
        `BC:    t = ccc;
        `BV:    t = ccv;
        `BLT:   t = ccn^ccv;
        `BLE:   t = (ccn^ccv) | ccz;
        `BLTU:  t = ~ccz&~ccc;
        `BLEU:  t = ccz | ~ccc;
    endcase
    br = hit & `BX & (cond[0] ? ~t : t);
end
```

Jumps and Branches

- Next PC is one of:
 - `i_ad_rst` on reset
 - `PC` $\sim hit \Rightarrow$ cache miss / no instruction; try to rerun current instruction
 - `PC+2` linear execution or branch not taken
 - `PC+2*disp` taken branch
 - `sum` `jal` (jump and link)

Jumps, Branches, Instruction Fetch

```
// jumps, branches, instruction fetch
wire [6:0]  sxd7   = {7{disp[7]}};
wire [`N:0] sxd16  = {sxd7, disp, 1'b0};
wire [`N:0] pcinc  = br ? sxd16 : {hit, 1'b0};

wire [`N:0] pcincd = pc + pcinc;
assign i_ad  = (hit & `JAL) ? sum : pcincd;

always @(posedge clk)
  if (rst)
    pc <= i_ad_rst;
  else if (valid_insn_ce)
    pc <= i_ad;
```

Instruction Fetch, cont'd

- Await rdy during valid loads and stores

```
wire mem      = hit & (`LB|`LW|`SB|`SW);  
assign insn_ce = rst | ~(mem & ~rdy);
```

- Another technology mapping optimization

```
i_ad = jal ? sum : (pc + pcinc);
```

- 4 inputs per bit => 1 4-LUT per bit
- Folding in the ?: mux saves 50% of LUTs
- (So far) synthesis tools miss these

Load/Store Data

■ Examples

```
sw r2,2(r3) ; mem[2+r3] = r2
```

```
lw r4,4(r5) ; r4 = mem[4+r5]
```

■ Verilog

```
// data loads, stores
```

```
assign d_ad = sum;
```

```
assign do = dreg;
```

```
assign lw = hit & `LW;
```

```
assign lb = hit & `LB;
```

```
assign sw = hit & `SW;
```

```
assign sb = hit & `SB;
```

Interrupt Support

- Inhibit interrupts in interlocked sequences
- Verilog


```
// interrupt support  
assign int_en = hit & ~(`IMM|`ALU&(`ADC|`SBC|`CMP));  
endmodule
```

- *Done!*

GR0041 Interruptible CPU Core

- Layer interrupts onto GR0040
- Hold request pending until `int_en` asserted
- Force `insn` to `jal r0, 2(r0)`
- Handler at 0002 takes request, then returns to `*r0`
- Just one CLB (or so)
- See paper for details

Simple SoC Logical Block Diagram

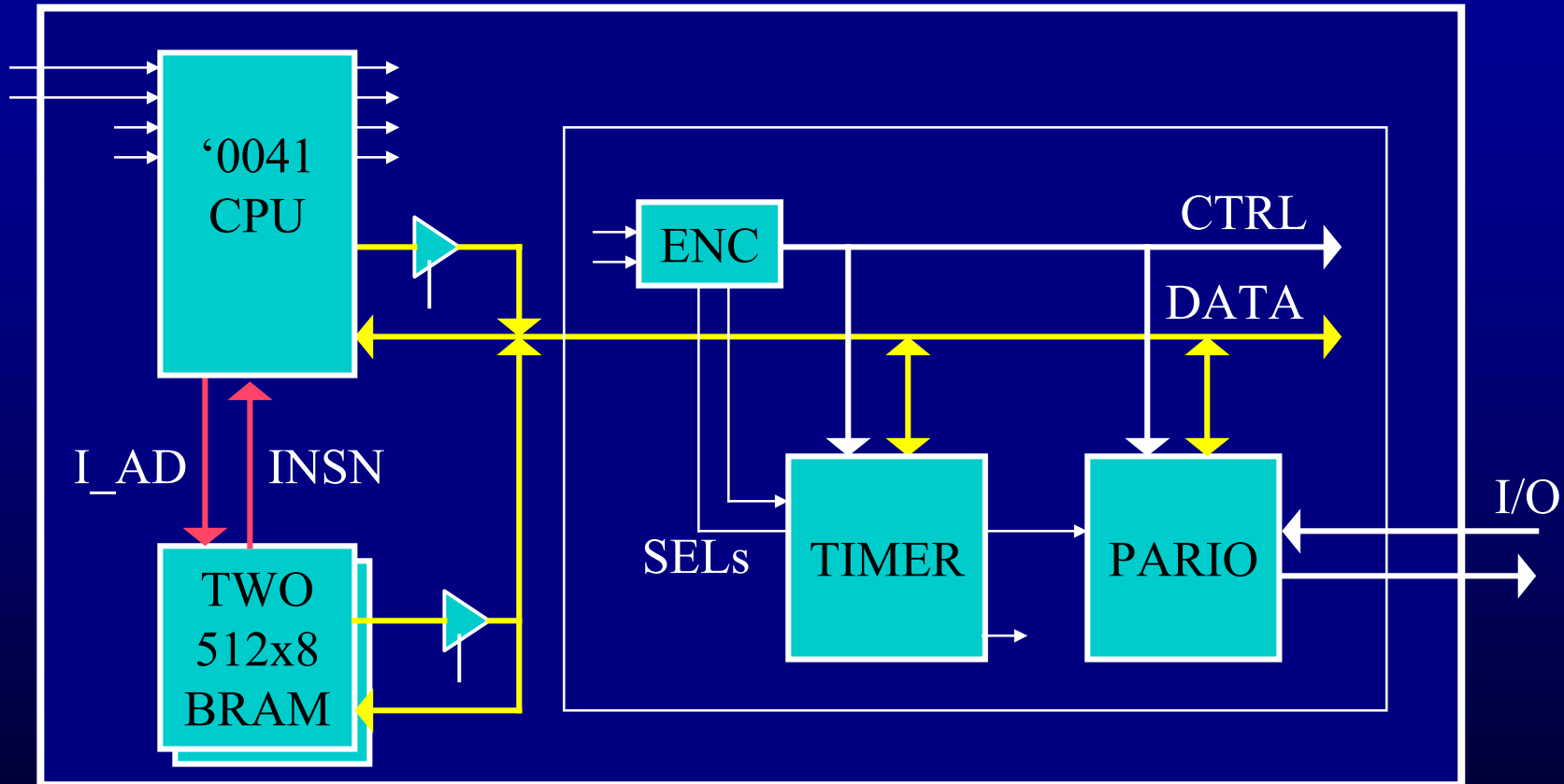

- Byte addressable 1 KB code and data storage
- Interrupt timer/counter and parallel I/O

System-On-Chip

...

```
module soc(clk, rst, par_i, par_o);  
    input  clk;           // clock  
    input  rst;          // reset (sync)  
  
    input  [7:0] par_i;  // parallel inputs  
    output [7:0] par_o;  // parallel outputs
```

Embedded Processor Core

// processor ports and control signals

```
wire [`AN:0] i_ad, d_ad;  
wire [`N:0]  insn, do;  
tri  [`N:0]  data;  
wire int_req, zero_insn;  
wire rdy, sw, sb, lw, lb;
```

```
gr0041 p(  
    .clk(clk), .rst(rst),  
    .i_ad_rst(16'h0020), .int_req(int_req),  
    .insn_ce(insn_ce), .i_ad(i_ad),  
    .insn(insn), .hit(~rst),  
    .zero_insn(zero_insn),  
    .d_ad(d_ad), .rdy(rdy),  
    .sw(sw), .sb(sb), .do(do),  
    .lw(lw), .lb(lb), .data(data));
```

Memory Control

- Decoding
 - 32 KB code and data RAM
 - 32 KB memory mapped I/O => 8 periph selects
- Wait states
 - Assert `rdy` unless selected peripheral is not ready
- Byte lane enables

Embedded RAM

■ Ideas

- 16-bits, byte addressable – RMW?
- Trade off code vs. data storage
- Each BRAM port can be 256x16, 512x8, ...

■ 2 BRAMs: ramh & raml

- Each with 512x8 instruction and data ports
- On byte stores, deassert one write enable
- Byte lane muxes => TBUFs
- *Boot RAM*

■ Expandable

Embedded RAM, cont'd

```
...
// embedded RAM
wire h_we = ~rst&~io_nxt&(sw|sb&~d_ad[0]);
wire l_we = ~rst&~io_nxt&(sw|sb&d_ad[0]);
wire [7:0] do_h = sw ? do[15:8] : do[7:0];
wire [`N:0] di;

RAMB4_S8_S8 ramh(
    .RSTA(zero_insn), .WEA(1'b0),
    .ENA(insn_ce), .CLKA(clk),
    .ADDRA(i_ad[9:1]), .DIA(8'b0), .DOA(insn[15:8]),

    .RSTB(rst), .WEB(h_we), .ENB(1'b1), .CLKB(clk),
    .ADDRB(d_ad[9:1]), .DIB(do_h), .DOB(di[15:8]));

RAMB4_S8_S8 raml(...);
```

Some FPGA On-Chip Buses

■ Contenders

- AMBA: ARM, Altera, LEON-1
 - APB? ASB? AHB?
- CoreConnect: IBM, Xilinx
- Wishbone: Silicore, OpenCores.org

■ Non-contenders ☺

- XSOC

XSOC On-Chip Bus

- Simple 16-bit on-chip data bus using TBUFs
- Bus/memory controller
 - Address decoding, bus controls (output enables, clock enables), RAM controls
- Make core reuse easy: *no glue logic required*
 - Abstract control signal bus
 - Encoded in SoC controller
 - Locally decoded within each core
 - Just add core, attach data, control, and select lines
 - Add features without invalidating designs or cores

Control, Select Bus Encoding

```
// control, sel bus encoding  
wire [`CN:0] ctrl;  
wire [`SELN:0] sel;  
ctrl_enc enc(  
    .clk(clk), .rst(rst), .io(io), .io_ad(io_ad),  
    .lw(lw), .lb(lb), .sw(sw), .sb(sb),  
    .ctrl(ctrl), .sel(sel));  
  
wire [`SELN:0] per_rdy;  
assign io_rdy = | (sel & per_rdy);
```

Using Peripherals

```
timer timer(  
    .ctrl(ctrl), .data(data),  
    .sel(sel[0]), .rdy(per_rdy[0]),  
    .int_req(int_req), .i(1'b1),  
    .cnt_init(16'hFFC0));
```

```
pario par(  
    .ctrl(ctrl), .data(data),  
    .sel(sel[1]), .rdy(per_rdy[1]),  
    .i(par_i), .o(par_o));
```

...

```
endmodule // soc
```

8-bit Parallel I/O (1)

```
// 8-bit parallel I/O peripheral
module pario(ctrl, data, sel, rdy, i, o);
  // XSOC boilerplate
  input  [`CN:0] ctrl;
  inout  [`DN:0] data;
  input  sel;
  output rdy;

  // parallel I/O
  input  [7:0] i;
  output [7:0] o;
  reg    [7:0] o;
```

8-bit Parallel I/O (2)

```
// xsoc boilerplate
wire clk;
wire [3:0] oe, we;
ctrl_dec d(.ctrl(ctrl), .sel(sel),
           .clk(clk), .oe(oe), .we(we));
assign rdy = sel;

// parallel port specific
always @(posedge clk)
    if (we[0])
        o <= data[7:0];
assign data[7:0] = oe[0] ? i[7:0] : 8'bz;
endmodule
```

16-bit Timer/Counter

- Timer: count when enabled
- Counter: count rising edges when enabled
- Interrupt on count overflow
- Memory mapped control registers
 - CR#0: struct { timer : 1; int_en : 1 };
 - CR#1: struct { irq : 1 };
- See paper for Verilog source

Outline

- Introduction
- FPGA Architecture
- Design of CPU and SoC
 - RISC CPU core
 - System-on-a-chip and peripherals
- Results, comparisons
- Software tools
- Conclusions

Synthesis results


- “Push button”
 - Synplify, Xilinx Alliance 3.1i
 - Complete rebuild in one minute
 - 2 BRAMs, 257 LUTs, 71 FFs, 130 TBUFs
 - 10% of Spartan-II-100, 27 ns cycle time (TRCE)
- Apply tech mapping and floorplanning to source
 - `/*synthesis xc_map="lut"*/`
 - `/*synthesis xc_props="RLOC=R1C0"*/`
 - 2 BRAMS + ~180 LUTs (8x6 CLBs)
 - ~20 ns cycle time

Comparisons

Core	Data width	Logic cells	Freq (MHz)
KCPSM	8	35 CLBs = 140 LCs?	35
gr0040	16	200	50
xr16	16	300	65
Nios	16	1100 LEs	50
gr0050 <i>hyp</i>	32	330 <i>est</i>	?
Nios	32	1700 LEs	50
ARC basecase	32	1538 slices = 3000+ LCs?	37

Chip Multiprocessors

 - 8 gr0040s in one small 16x24 CLB XCV50E
 - Each 8x6 CLBs, 2 BRAMs
 - Each with 1 KB shared local program/data RAM



Achilles Heel: Software Tools

- CPU core is much easier than the compiler
- Retargetable C compilers
 - LCC, *Fraser and Hanson*
 - GCC
- Assemblers, linkers, C libs, debuggers, RTOS ...
 - Here GCC shines
 - Nios

Porting LCC

- Download from cs.princeton.edu/software/lcc
 - `mips.md` \Rightarrow `gr0040.md`
 - 32 registers \Rightarrow 16 registers
 - `sizeof(int)==sizeof(void*)==4` \Rightarrow 2
 - Misc: branches; long ints; software mul/div
- Assembler
 - Lex, parse, fix far branches, apply fixups, emit
 - “Link in the assembler”
- Instruction set simulator
- Alas no C runtime library

LCC Generated Code

```
■ typedef struct TN {  
    int k;  
    struct TN *left, *right;  
} *T;
```

```
T search(int k, T p) {  
    while (p && p->k != k)  
        if (p->k < k)  
            p = p->right;  
        else  
            p = p->left;  
    return p;  
}
```

```
■ _search:                ; r3=k r4=p  
    br L3  
L2: lw r9,(r4)  
    cmp r9,r3             ; p->k < k?  
    bge L5  
    lw r4,4(r4)          ; p=p->right  
    br L6  
L5: lw r4,2(r4)          ; p=p->left  
L6:  
L3: mov r9,r4  
    cmp r9,r0             ; p==0?  
    beq L7  
    lw r9,(r4)  
    cmp r9,r3             ; p->k != k?  
    bne L2  
L7: mov r2,r4            ; retval=p  
L1: ret
```

Compact Soft CPU Core Applications

- Trade off software for hardware, for shorter TTM
- Interface to outside world: protocol mgmt, UIs
- Custom datapaths and coprocessors
- Absorbing a discrete MCU
- Ephemeral self test

Recap / Conclusions

- It's easy to build an FPGA SoC
 - KISS and save: CPU <\$1 of programmable logic
- Design for the FPGA
 - Know and use the device primitives
 - 4-LUTs, carry, FF clock enables, TBUFs, BRAM ports, ...
 - *4-LUTs 4-LUTs 4-LUTs*
 - Review the synthesized netlist
 - Study the static timing analysis report
 - Explicitly map and floorplan key datapaths
- Soft CPUs prominent in the Platform FPGA future

Resources

■ Online

- comp.arch.fpga; www.fpgacpu.org;
fpga-cpu@egroups.com

■ FPGAs

- www.xilinx.com
- Trimmerger, S., *Field-Programmable Gate Array Technology*.

■ LCC

- C. Fraser and D. Hanson, *A Retargetable C Compiler: Design and Implementation*.

■ RISC architecture/implementation


- D. Patterson and J. Hennessy, *Computer Organization and Design: The Hardware/Software Interface*

Designing a Simple FPGA-Optimized RISC CPU and System-on-a-Chip

Jan Gray, Gray Research LLC

`jsgray@acm.org`

`www.fpgacpu.org`

 

`lw r12,4(r3)`

Copyright © 2001, Gray Research LLC. All Rights Reserved.