

Q1

a)

129/2	64	1
64/2	32	0
32/2	16	0
16/2	8	0
8/2	4	0
4/2	2	0
2/2	1	0
1/2	0	1

b)

1001	0111
1001	1000
10010	1111
0110	0110
0001	1001
	0101

← Not BED number
add 0110 to both numbers

Answer $129_{10} = 10000001_2$
 $8 : 1 = 8_{16}$

Answer 0001 1001 0101


Q2

a) $[\overline{xy} \cdot (x + \overline{y}) + xy \cdot (x + \overline{y})] \cdot [W(W + Y) + \overline{W} \cdot \overline{(W + Y)}]$
 $[(\overline{x} \overline{y}) \cdot (x + \overline{y}) + xy \cdot (x + \overline{y})] \cdot [W + \overline{W} \cdot \overline{(W + Y)}]$
 $[(\overline{x} + \overline{y})(x + \overline{y}) + xy(\overline{x} + \overline{y})] \cdot [W + \overline{W} \cdot \overline{y}]$
 $[\overline{x}x + \overline{x}\overline{y} + x\overline{y} + \overline{y} + x\overline{x}y] \cdot [W + \overline{y}]$
 $[0 + \overline{y}] \cdot [W + \overline{y}] = \overline{y}$

b) There are 3, paths to the output. The longest path is \Rightarrow $\overline{D} \xrightarrow{8ns} D \xrightarrow{4ns} \overline{D} \xrightarrow{10ns} D$
 Delay is equal to $d = 8 + 4 + 10 = 22 \text{ ns}$ $f = \frac{10^9}{22} = 45.45 \text{ MHz}$

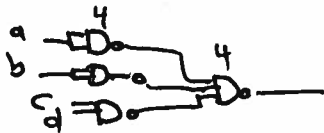c) $(a \oplus b) \cdot \overline{cd} + a = \overline{\overline{a \oplus b + \overline{cd} + a}} = \overline{\overline{a \oplus b} + \overline{cd} + a}$
 $= \overline{\overline{a} \overline{b} + \overline{a} b + a + \overline{cd}}$
 $= \overline{\overline{a} \overline{b} + a + \overline{cd}}$
 $= a + b + cd$



Maximum frequency is obtained by a NAND-NAND Implementation



total delay = 4 + 4 = 8 ns

Maximum frequency = $\frac{10^9}{8} = 125 \text{ MHz}$

Q2

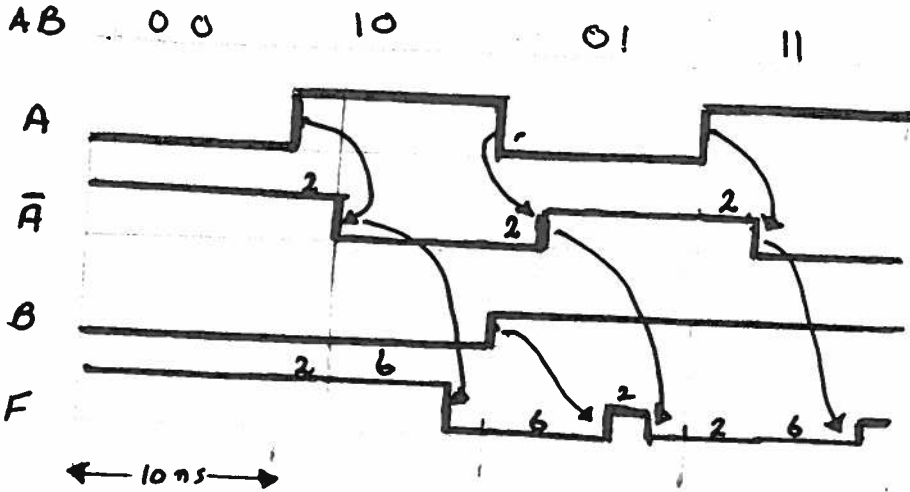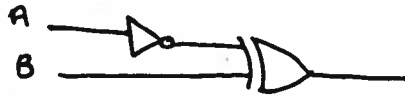

Q4

4.a)

$$EPI_1 = \sum m(0, 2, 4, 6, 8, 10, 12, 14) = \bar{d}$$

$$EPI_2 = \sum m(2, 3, 10, 11) = \bar{b}c$$

$$EPI_3 = \sum m(4, 5, 12, 13) = b\bar{c}$$

Minimum $F = EPI_1 + EPI_2 + EPI_3 = \bar{d} + \bar{b}c + b\bar{c}$

4.a

	ab	00	01	11	10
cd	00	1	X	X	X
	01				
	11	1			1
	10	X	X	X	X

4.b) $F(A, B, C, D) = (A+CD)(B+CD) = (A+C)(A+D)(B+C)(B+D)$

4.c) $F(A, B, C, D) = B = \sum m(4, 5, 6, 7, 12, 13, 14, 15)$

4.c

	AB	00	01	11	10
CD	00		1	1	
	01			1	
	11		1	1	
	10		1	1	

4.d) From Kmap 4.d

$$F = A(c+d)(b+d)$$

$$= \overline{A \cdot (c+d) \cdot (b+d)}$$

$$= \overline{A} + \overline{(c+d)} + \overline{(b+d)}$$

Double Negate

4.d

	AB	00	01	11	10
CD	00	0	0	0	0
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	1	1

